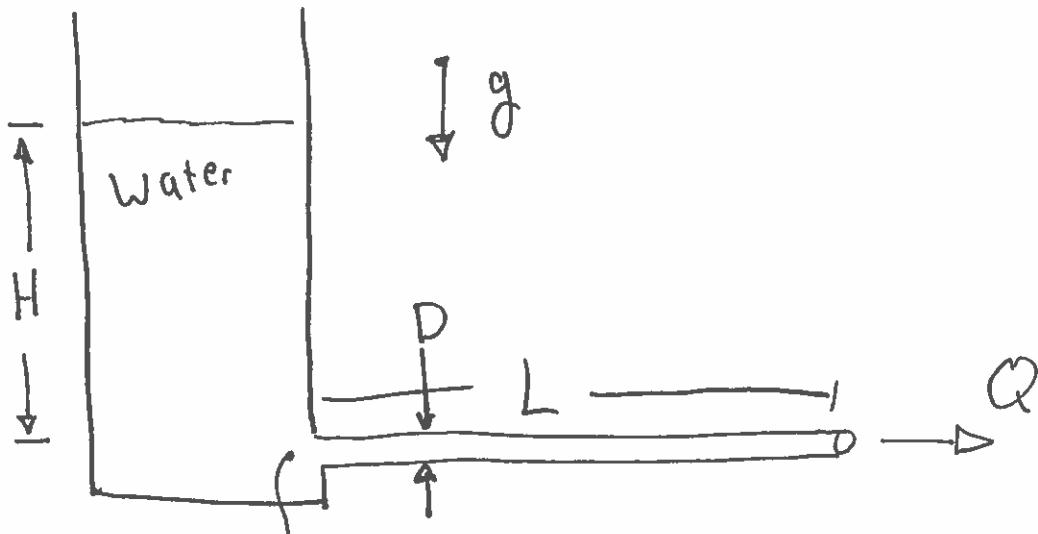


①



Pressure here is $\rho g H$ where
 ρ is density of water.

Q is volumetric flow rate

Q is measured in m^3/second .


Note that pressure increases as depth, H , increases.

What do we expect?

- Higher pressure (deeper water) \Rightarrow Higher flow
- Increase in pipe length or decrease its diameter will result in lower flow.

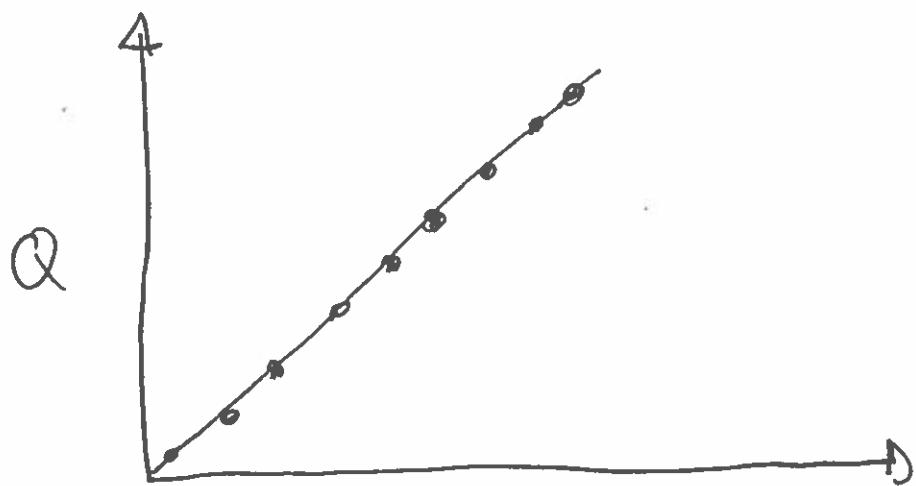(2)

Imagine an experiment where we adjust the height of water in the tank and measure the resulting flow. We can plot the data as:



$$P = \rho g H$$

Imagine data follows straight line.

Define Resistance as:


$$R = \frac{P}{Q}$$

-OR-

$$P = QR$$

When R is a constant, we have a simple law to predict flow - Pressure relation.

(3)

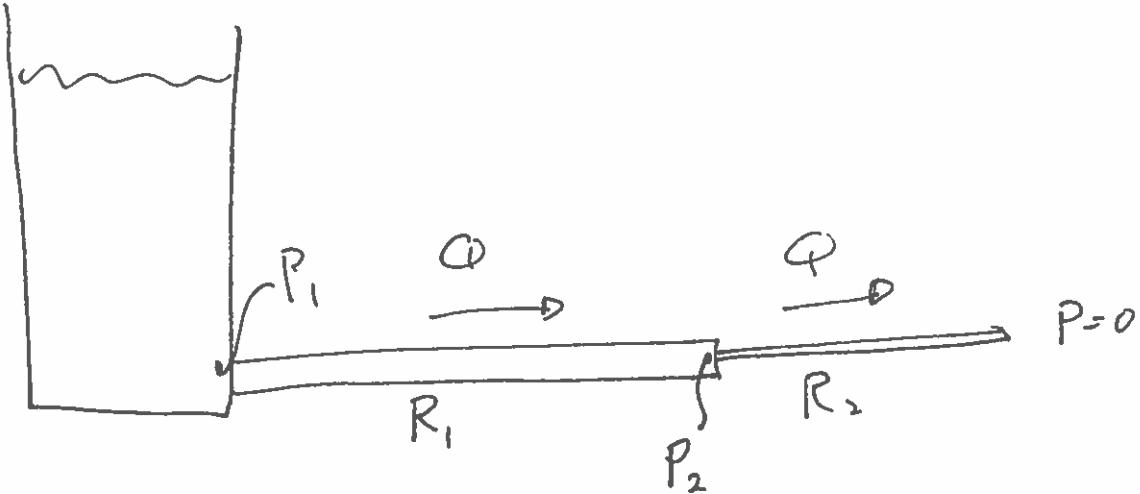

Two pipes in series

Resistance of each is known.

$$\textcircled{a} \quad (P_1 - P_2) = Q R_1 \quad \left. \begin{array}{l} \\ P_2 = Q R_2 \end{array} \right\} \text{Holds for each pipe.}$$

Add the equations.

$$P_1 - P_2 + P_2 = Q R_1 + Q R_2$$


$$\boxed{P_1 = Q(R_1 + R_2)}$$

Note that the piping system has a total resistance

of $R_{\text{equivalent}} = R_1 + R_2$

The resistances add up.

(4)

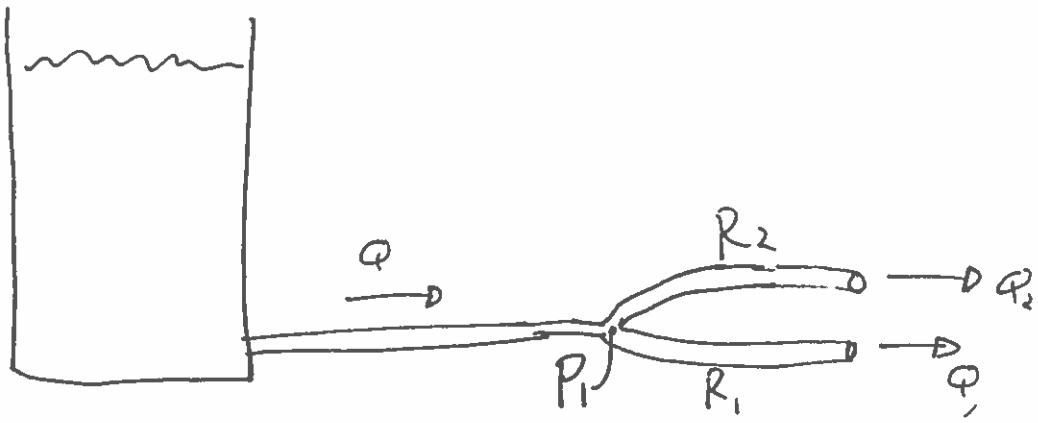

Imagine pipe splitting. $Q_1 + Q_2 = Q$

Relationship must hold if amount of water is conserved.

Intuitively if $R_1 >> R_2$ then most of flow goes through pipe #2.

Relations for this system are:

$$P_1 = Q_1 R_1$$

$$P_1 = Q_2 R_2$$

$$Q = Q_1 + Q_2$$

Making Substitutions


$$Q = \frac{P_1}{R_1} + \frac{P_1}{R_2} = P_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$P_1 = Q \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right)$$


equivalent
resistance.

(5)

Analogy to electrical circuits

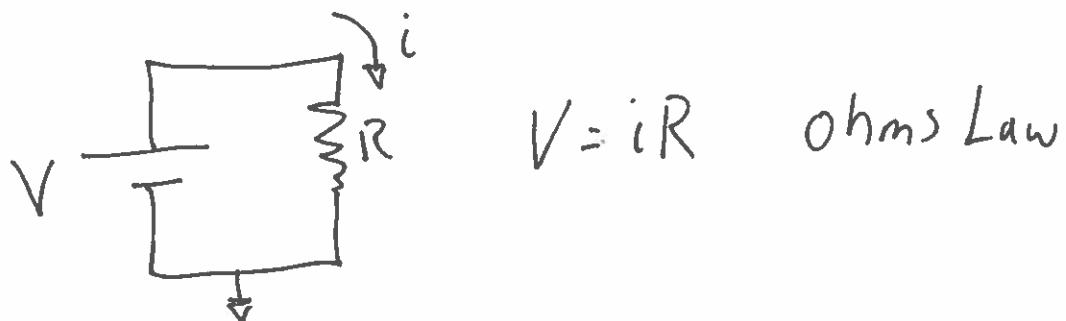

$$V = iR \quad \text{Ohms Law}$$

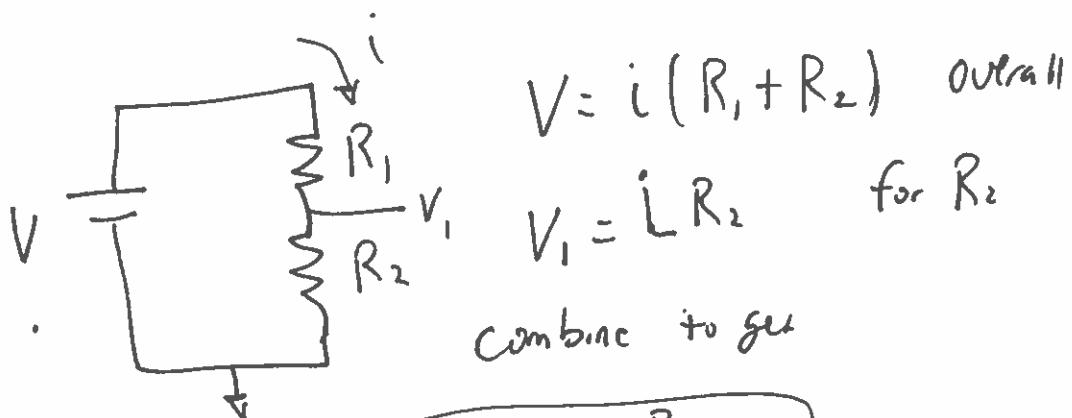

$$V = i(R_1 + R_2) \quad \text{overall}$$

$$V_1 = iR_2 \quad \text{for } R_2$$

combine to get

$$V_1 = V \frac{R_2}{R_1 + R_2}$$

Voltage
divider.


If $R_1 \gg R_2$ $V_1 \Rightarrow 0$

If $R_2 \gg R_1$ $V_1 \Rightarrow V$

If $R_1 = R_2$ $V_1 = \frac{V}{2}$

(6)

Resistors in Parallel

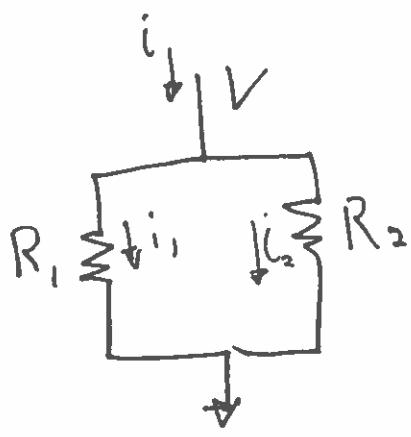

$$i_1 + i_2 = i$$

$$V = i_1 R_1$$

$$V = i_2 R_2$$

Combining gives

$$i = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Rearrange to get

$$V = i \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right) \quad \text{Equivalent Resistance}$$

Can write as

$$V = i \left(\frac{R_1}{1 + R_1/R_2} \right)$$

When $R_2 \gg R_1$ equivalent $R \rightarrow R_1$