

Euler Identity

$$e^{j\theta} = \cos\theta + j\sin\theta$$

Proof

Taylor series for e^x

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \frac{x^5}{5!} + \frac{x^6}{6!} + \dots$$

So


$$e^{j\theta} = 1 + j\theta - \frac{\theta^2}{2!} - j\frac{\theta^3}{3!} + \frac{\theta^4}{4!} + j\frac{\theta^5}{5!} - \frac{\theta^6}{6!} - j\frac{\theta^7}{7!} + \dots$$

$$e^{j\theta} = \left(1 - \frac{\theta^2}{2!} + \frac{\theta^4}{4!} - \frac{\theta^6}{6!} + \dots\right) + j\left(\theta - \frac{\theta^3}{3!} + \frac{\theta^5}{5!} - \frac{\theta^7}{7!} + \dots\right)$$

$$e^{j\theta} = \cos\theta + j\sin\theta$$

\Downarrow Taylor Series \leftarrow Taylor Series

Plots in Complex plane

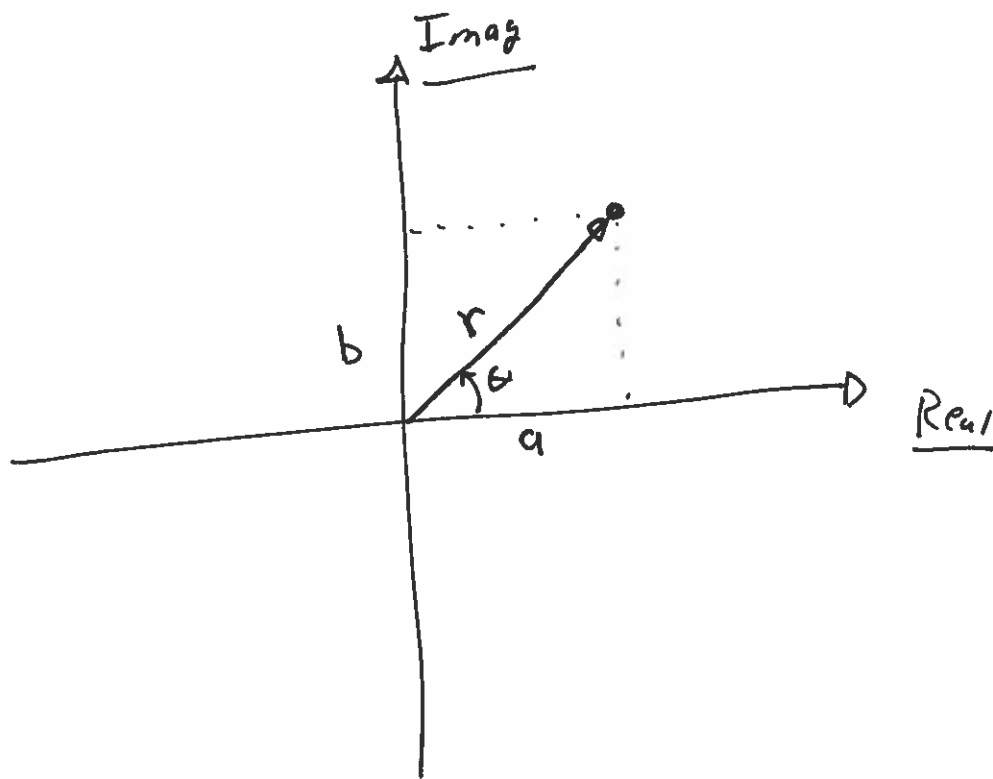

Complex # is: $a + bj$

$$r = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1}\left(\frac{b}{a}\right)$$

$$a = r \cos \theta$$

$$b = r \sin \theta$$

So

$$a + bj = r \cos \theta + j r \sin \theta = r e^{j\theta}$$

Let's assume we can represent a time varying, sinusoidal voltage as

$$V(t) = \mathbb{V} e^{j\omega t}$$

where $\mathbb{V} = a + bj$ is a complex amplitude
 ω is the frequency, $r = \sqrt{a^2 + b^2}$

Connection to Sines/Cosines

$$V(t) = (a + bj) (\cos \omega t + j \sin \omega t)$$

$$V(t) = (a \cos \omega t - b \sin \omega t) + j (b \cos \omega t + a \sin \omega t)$$

$$V(t) = r \left(\frac{a}{r} \cos \omega t - \frac{b}{r} \sin \omega t \right) + j r \left(\frac{b}{r} \cos \omega t + \frac{a}{r} \sin \omega t \right)$$


$$V(t) = r (\cos \theta \cos \omega t - \sin \theta \sin \omega t) + j r (\sin \theta \cos \omega t + \cos \theta \sin \omega t)$$

⇓ trig identities

$$V(t) = r \cos(\omega t + \theta) + j r \sin(\omega t + \theta)$$

So putting $V(t) = \mathbb{V} e^{j\omega t}$ is equivalent to using sines + cosines. The magnitude of $|\mathbb{V}| = \sqrt{a^2 + b^2} = r$ is the amplitude.

Example

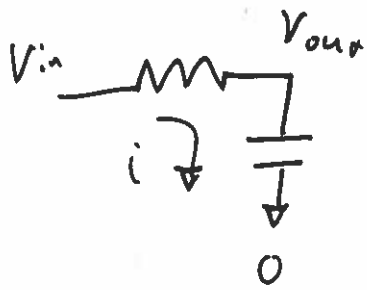

$$i = \frac{V_{in} - V_{out}}{R} = C \frac{dV_{out}}{dt}$$

$$RC \frac{dV_{out}}{dt} = V_{in} - V_{out}$$

assume $V_o(t) = V_o e^{j\omega t} = |V_o| \left(\cos(\omega t + \theta) + j \sin(\omega t + \theta) \right)$
 $V_{in}(t) = V_{in} e^{j\omega t} = |V_{in}| \left(\cos(\omega t + \theta) + j \sin(\omega t + \theta) \right)$

$$RC j\omega V_o e^{j\omega t} = V_{in} e^{j\omega t} - V_o e^{j\omega t}$$

$e^{j\omega t}$ cancels


$$(RC j\omega + 1) V_o = V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + RC j\omega} = \frac{1}{1 + RC j\omega} \frac{1 - RC j\omega}{1 - RC j\omega}$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{1 - RC j\omega}{1 + (RC\omega)^2}}$$

Let's assume

$$V_{in} = 1$$

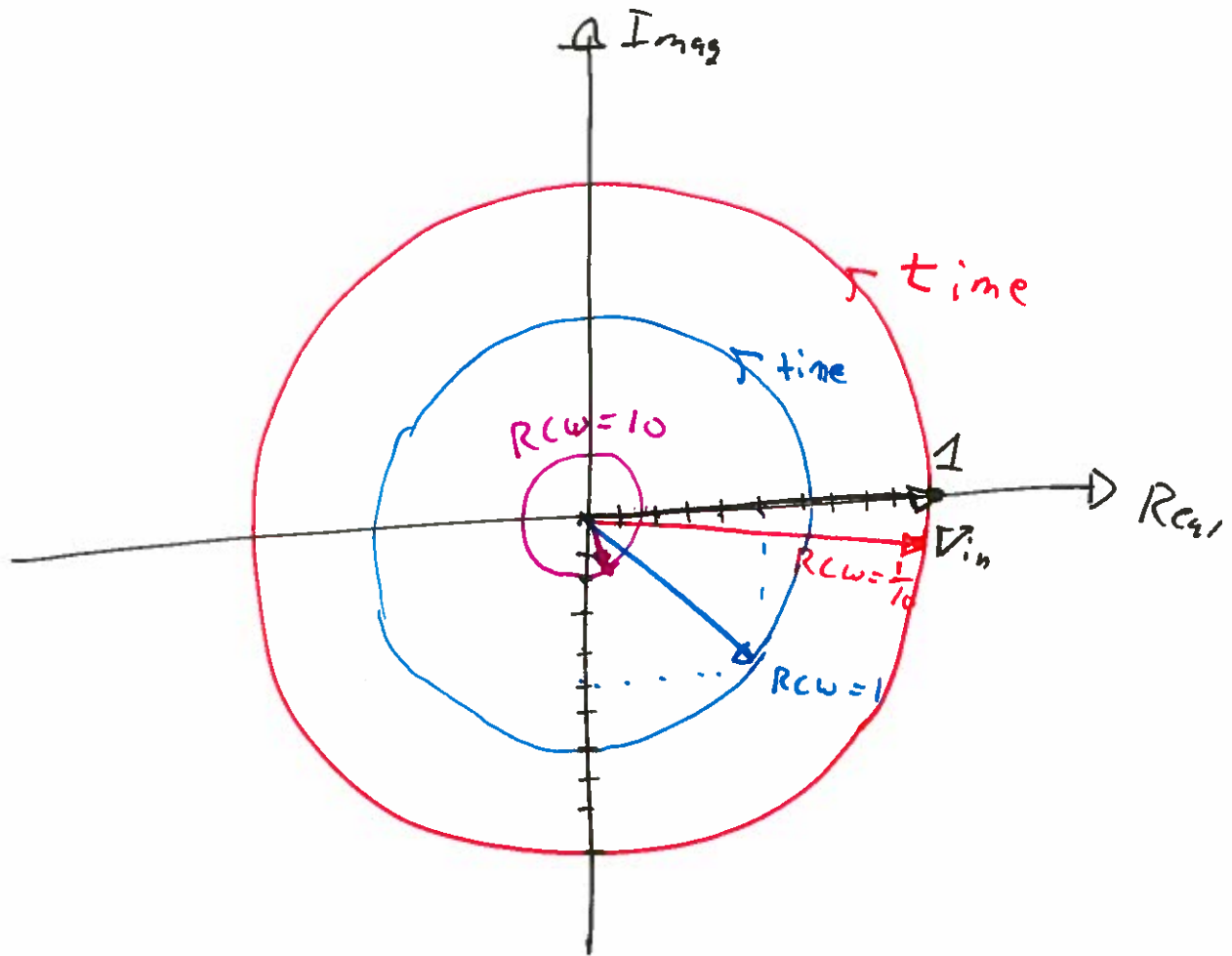

Cases

$$RCW = \frac{1}{10} \Rightarrow V_{out} = \frac{1 - \frac{j}{10}}{1.01} = \frac{1}{1.01} - \frac{j}{(1.0) \cdot (1.0)}$$

$$RCW = 1 \Rightarrow V_{out} = \frac{1 - j}{2} \quad |V_o| = \frac{1}{\sqrt{2}}$$

$$RCW = 10 \Rightarrow V_{out} = \frac{1 - 10j}{1 + 10^2} = \frac{1}{101} - \frac{10j}{101}$$

Analytically

$$\vec{V}_o = \frac{1 - RC\omega j}{(1 + (RC\omega)^2)}$$

$$|\vec{V}_o| = \sqrt{\frac{1}{(1 + (RC\omega)^2)^2} + \frac{(RC\omega)^2}{(1 + (RC\omega)^2)^2}}$$

$$= \sqrt{\frac{1 + (RC\omega)^2}{(1 + (RC\omega)^2)^2}}$$

Derived in earlier course notes

$$|\vec{V}_o| = \sqrt{\frac{1}{1 + (RC\omega)^2}}$$


Imag Part!

$$\Theta = \text{atan} \left(\frac{-\frac{RC\omega}{1 + (RC\omega)^2}}{\frac{1}{1 + (RC\omega)^2}} \right) = \text{atan}(-RC\omega)$$

Real Part!

Same result as before

Impedance

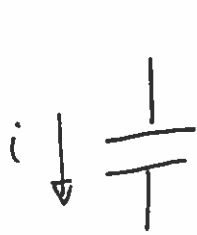

$$V(t) = V e^{j\omega t}$$

$$i = C \frac{dV}{dt}$$


$$i = CV j\omega e^{j\omega t}$$

So


$$\frac{V(t)}{i(t)} = \frac{V e^{j\omega t}}{CV j\omega e^{j\omega t}} = \frac{1}{j\omega C} = Z \text{ (impedance)}$$

- By definition we take the ratio of Voltage and current to be the impedance
- It turns out using impedances we can analyze circuits just like it was resistors.


Examples

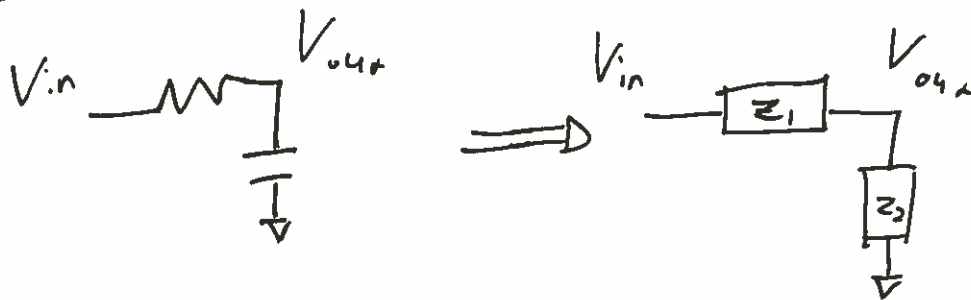
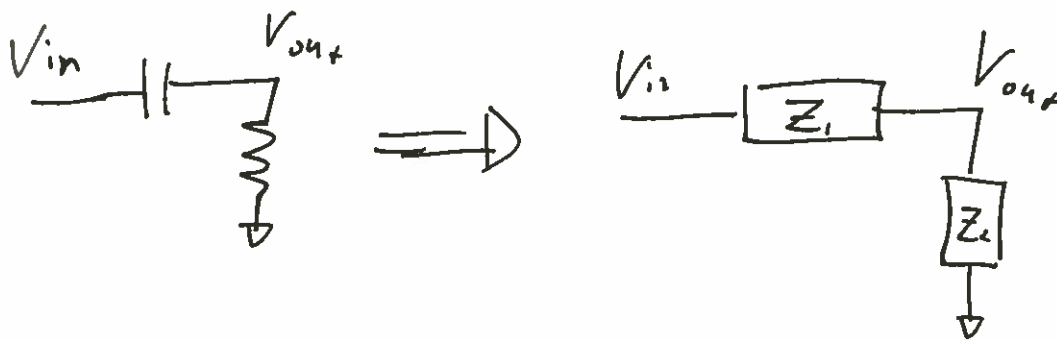
$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{1/j\omega C}{R + 1/j\omega C} = \boxed{\frac{1}{1 + j\omega RC}}$$


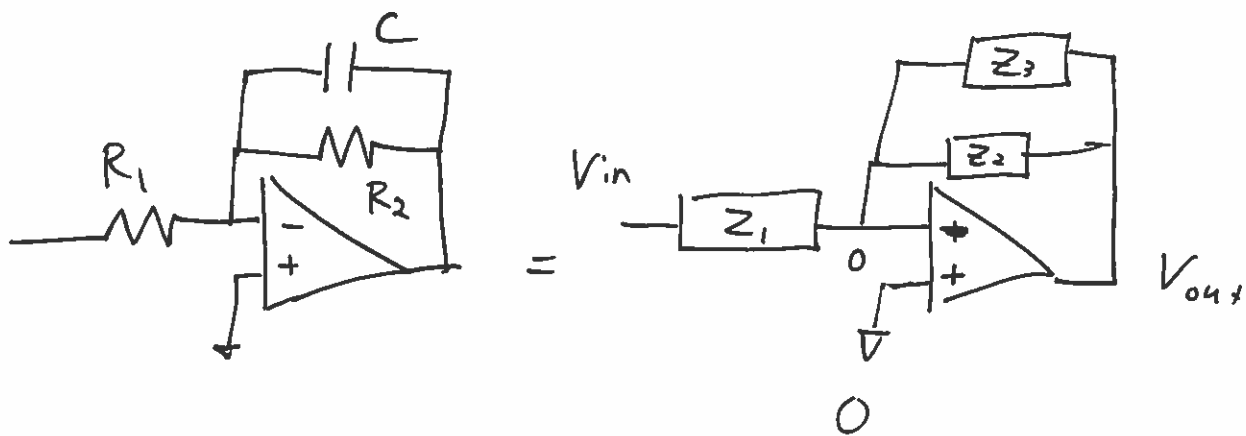
$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{R}{R + 1/j\omega C} = \boxed{\frac{j\omega RC}{1 + j\omega RC}}$$



Same analysis as with resistors.

$$i_1 = \frac{V_{in}}{Z_1} \quad i_2 = \frac{-V_{out}}{Z_2} \quad i_3 = \frac{-V_{out}}{Z_3}$$

$$i_1 = i_2 + i_3$$

$$\frac{V_{in}}{Z_1} = -V_{out} \left(\frac{1}{Z_2} + \frac{1}{Z_3} \right)$$

$$\frac{V_{out}}{V_{in}} = - \frac{\frac{1}{Z_1}}{\frac{1}{Z_2} + \frac{1}{Z_3}} = \frac{-\frac{1}{R_1}}{\frac{1}{R_2} + j\omega C}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{-R_2/R_1}{1 + j\omega C R_2}}$$