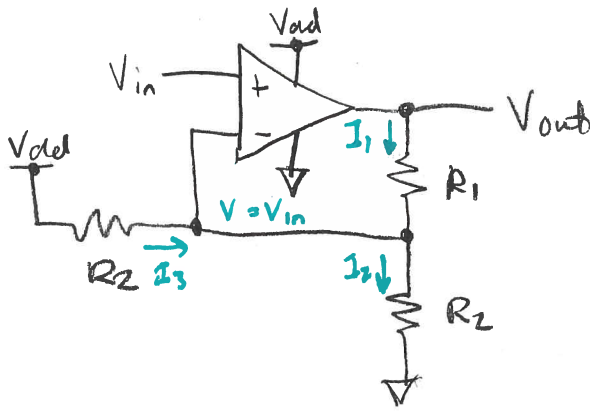


①



$0V < V_{out} < V_{dd} \Rightarrow V \approx V_{in}$

KCL @ V $\Rightarrow I_1 + I_3 = I_2$

$$\Rightarrow \underbrace{\frac{V_{out} - V_{in}}{R_1}}_{I_1} + \underbrace{\frac{V_{dd} - V_{in}}{R_2}}_{I_3} = \underbrace{\frac{V_{in} - 0V}{R_2}}_{I_2}$$

(=) $\times R_1 \Rightarrow V_{out} = \left(1 + 2\frac{R_1}{R_2}\right) V_{in} - \frac{R_1}{R_2} V_{dd}$


(=) $-\frac{V_{dd}}{2} \Rightarrow$

$$V_{out} - \frac{V_{dd}}{2} = \left(1 + 2\frac{R_1}{R_2}\right) V_{in} - \left(\frac{1}{2} + \frac{R_1}{R_2}\right) V_{dd}$$

$$\Rightarrow V_{out} - \frac{V_{dd}}{2} = \left(1 + 2\frac{R_1}{R_2}\right) V_{in} - \left(1 + 2\frac{R_1}{R_2}\right) \frac{V_{dd}}{2}$$

$$\Rightarrow \underbrace{V_{out} - \frac{V_{dd}}{2}}_{U_{out}} = \underbrace{\left(1 + 2\frac{R_1}{R_2}\right)}_A \underbrace{\left(V_{in} - \frac{V_{dd}}{2}\right)}_{U_{in}}$$

②

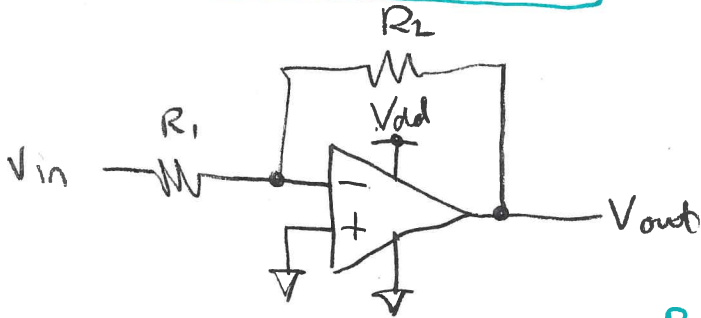

Inverting amplifier, Gain = $-\frac{R_2}{R_1}$, $V_{ref} = 0V$.

Expect $V_{out} = -\frac{R_2}{R_1} V_{in}$. However, V_{out} can't go below $0V$!


If $V_{in} > 0V$, V_{out} wants to go below $0V$, but gets stuck at $0V$.

So, if V_{in} can go below ground, the circuit's response will look like this



If the input range were limited to positive voltages, the output will always be stuck at $0V$!

③

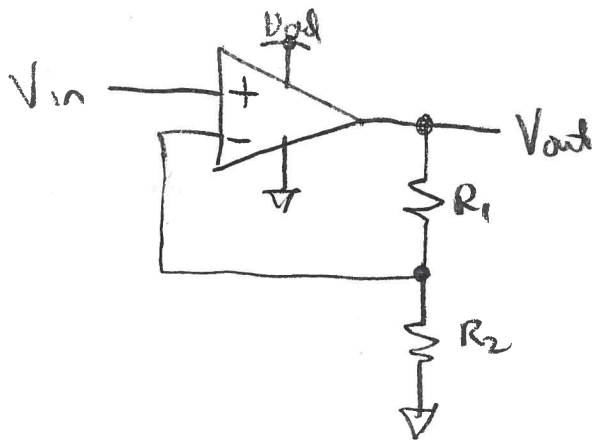


Noninverting amp with $V_{ref} = 0V$

$$V_{out} - 0V = \left(1 + \frac{R_1}{R_2}\right)(V_{in} - 0V)$$

$$\Rightarrow V_{out} = \left(1 + \frac{R_1}{R_2}\right)V_{in}$$

until V_{out} saturates @ V_{sat}

④

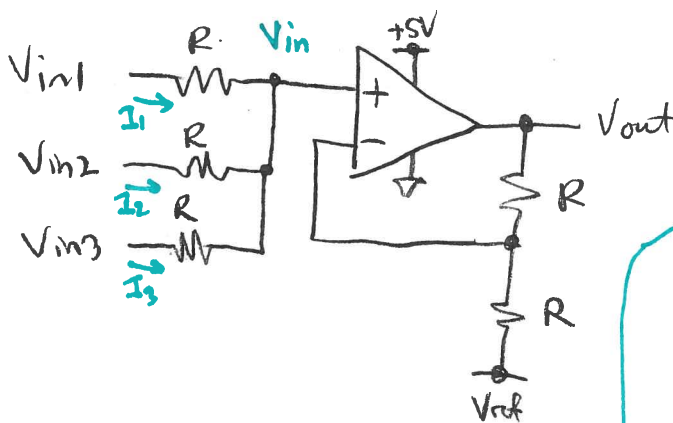

Noninverting amp w/ $R_1 = R_2 = R$.

$$\Rightarrow A = 2.$$

$$\Rightarrow V_{out} - V_{ref} = 2(V_{in} - V_{ref})$$

$$\Rightarrow V_{out} - V_{ref} = 2\left(\frac{V_{in1} + V_{in2} + V_{in3}}{3} - V_{ref}\right)$$


$$\text{KCL @ } V_{in} \Rightarrow I_1 + I_2 + I_3 = 0A$$

$$\Rightarrow \underbrace{\frac{V_{in1} - V_{in}}{R}}_{I_1} + \underbrace{\frac{V_{in2} - V_{in}}{R}}_{I_2} + \underbrace{\frac{V_{in3} - V_{in}}{R}}_{I_3} = 0A.$$

$$(\cdot) \times R \Rightarrow V_{in1} + V_{in2} + V_{in3} = 3V_{in}$$

$$\Rightarrow V_{in} = \frac{1}{3}(V_{in1} + V_{in2} + V_{in3})$$

5

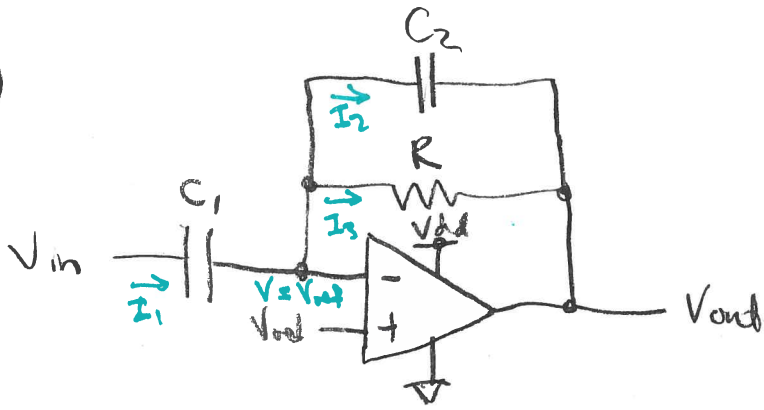

or $V_{out} < V_{ref} \Rightarrow V = V_{ref}$

$$I_1 = C_1 \frac{d}{dt} (V_{in} - V_{ref}),$$

$$I_2 = C_2 \frac{d}{dt} (V_{ref} - V_{out}),$$

and $I_3 = \frac{V_{ref} - V_{out}}{R}$

KCL @ V $\Rightarrow I_1 = I_2 + I_3$

$$\Rightarrow \underbrace{C_1 \frac{d}{dt} (V_{in} - V_{ref})}_{I_1} = \underbrace{C_2 \frac{d}{dt} (V_{ref} - V_{out})}_{I_2} + \underbrace{\frac{V_{ref} - V_{out}}{R}}_{I_3}$$

(=) $\times -R \Rightarrow -RC_1 \frac{d}{dt} (V_{in} - V_{ref}) = RC_2 \frac{d}{dt} (V_{out} - V_{ref}) + (V_{out} - V_{ref})$

$$\Rightarrow \underbrace{RC_2}_{\tau} \frac{d}{dt} \underbrace{(V_{out} - V_{ref})}_{U_{out}} + \underbrace{(V_{out} - V_{ref})}_{U_{out}} = \underbrace{-\frac{C_1}{C_2}}_A \cdot \underbrace{RC_2}_{\tau} \frac{d}{dt} \underbrace{(V_{in} - V_{ref})}_{U_{in}}$$

$$\tau \frac{dU_{out}}{dt} + U_{out} = A \tau \frac{dU_{in}}{dt}$$

First-order high-pass filter!

When $\tau = RC_2$

$$A = -\frac{C_1}{C_2}$$