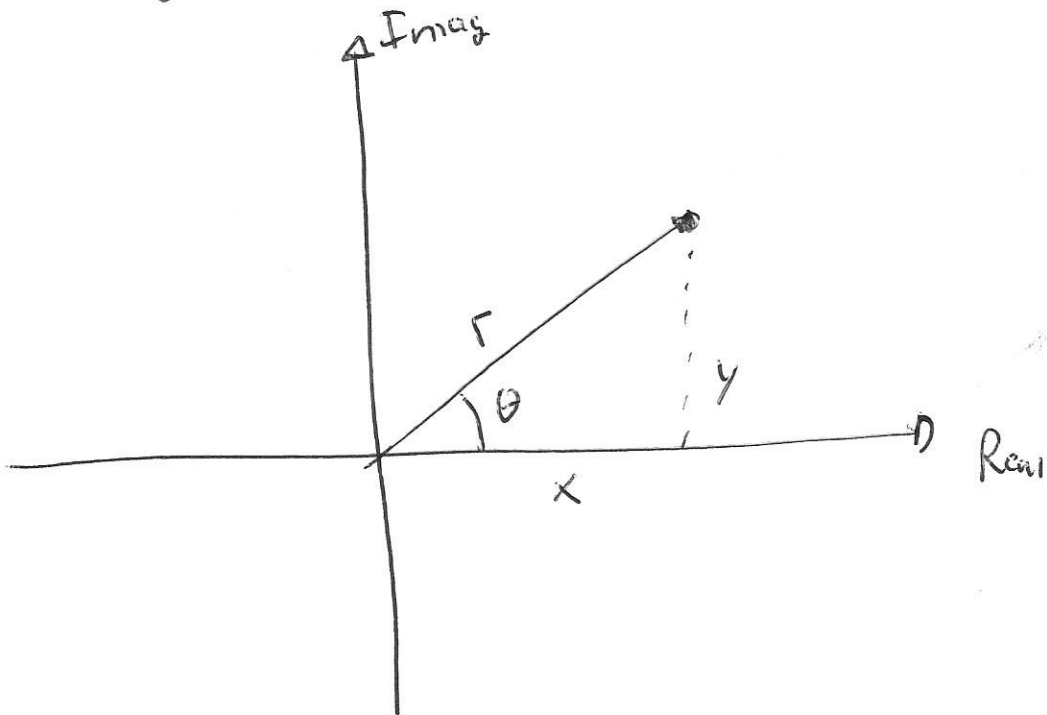


Complex Plane

$$Z = x + jy$$



$$r^2 = x^2 + y^2$$

$$\tan^{-1}\left(\frac{y}{x}\right) = \theta$$

$$Z = r \cos \theta + r \sin \theta j$$

Can give complex # Z as $Z = r \angle \theta$

Taylor Series

$$f(x) = f(0) + \left. \frac{df}{dx} \right|_{x=0} x + \left. \frac{d^2 f}{dx^2} \right|_{x=0} \frac{x^2}{2} + \left. \frac{d^3 f}{dx^3} \right|_{x=0} \frac{x^3}{3!} + \dots + \left. \frac{d^n f}{dx^n} \right|_{x=0} \frac{x^n}{n!}$$

Try for $f(x) = e^x$

where $\frac{d}{dx} e^x = e^x$; $\frac{d^2}{dx^2} e^x = e^x$

$$e^x = e^0 + e^0 x + e^0 \frac{x^2}{2} + e^0 \frac{x^3}{3!} + \dots + e^0 \frac{x^n}{n!}$$

$$e^x = 1 + x + \frac{x^2}{2} + \frac{x^3}{3!} + \dots + \frac{x^n}{n!}$$

Try $\cos(x)$

where $\frac{d}{dx} \cos(x) = -\sin(x)$ $\frac{d^2}{dx^2} = -\cos(x)$ $\frac{d^3}{dx^3} = \sin(x) \dots$

$$\cos x = \cos(0) - \sin(0)x - \cos(0) \frac{x^2}{2} + \sin(0) \frac{x^3}{3!} + \cos(0) \frac{x^4}{4!} + \dots$$

$$= 1 - 0 - \frac{x^2}{2} + 0 + \frac{x^4}{4!}$$

$$= 1 - \frac{x^2}{2} + \frac{x^4}{4!} - \frac{x^6}{6!} + \frac{x^8}{8!} + \dots$$

Try Sin(x)

$$\text{Where } \frac{d \sin(t)}{dt} = \cos t \quad \frac{d^2}{dt^2} = -\sin(t)$$

$$\begin{aligned} \sin x &= \sin(0) + \cos(0)x - \sin(0)\frac{x^2}{2} - \cos(0)\frac{x^3}{3!} \\ &= 0 + x - 0 - \frac{x^3}{3!} + \dots \\ &= x - \frac{x^3}{3!} + \frac{x^5}{5!} - \frac{x^7}{7!} + \dots \end{aligned}$$

Try e^{jx}

$$\frac{d}{dx} e^{jx} = j e^{jx} \quad \frac{d^2}{dx^2} = -e^{jx} \quad \frac{d^3}{dx^3} = -j e^{jx} \quad \frac{d^4}{dx^4} = e^{jx}$$

$$e^{jx} = e^{j \cdot 0} + j e^{j0} x - e^{j0} \frac{x^2}{2} - j e^{j0} \frac{x^3}{3!} + e^{j0} \frac{x^4}{4!} + j e^{j0} \frac{x^5}{5!} - e^{j0} \frac{x^6}{6!} + \dots$$


$$e^{jx} = 1 + jx - \frac{x^2}{2} - \frac{jx^3}{3!} + \frac{x^4}{4!} + j\frac{x^5}{5!} - \frac{x^6}{6!} + \dots$$

$$e^{jx} = \left(1 - \frac{x^2}{2} + \frac{x^4}{4!} - \frac{x^6}{6!} + \dots \right) + j \left(x - \frac{x^3}{3!} + \frac{x^5}{5!} + \dots \right)$$

$$e^{jx} = \cos x + j \sin x$$

Therefore

$$Z = x + jy$$

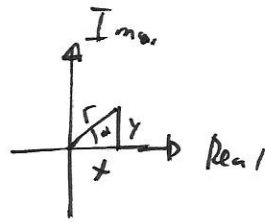

$$Z = r \cos \theta + j \sin \theta$$

$$Z = r (\cos \theta + j \sin \theta) = r e^{j\theta}$$

Complex multiplication

$$\begin{aligned} Z_1 \cdot Z_2 &= r_1 e^{j\theta_1} r_2 e^{j\theta_2} \\ &= r_1 r_2 e^{j(\theta_1 + \theta_2)} \end{aligned}$$

in polar form, multiplication is easy, angles add

Division

$$\frac{Z_1}{Z_2} = \frac{r_1 e^{j\theta_1}}{r_2 e^{j\theta_2}} = \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)}$$

angles subtract!

Let's assume a function

$$V(t) = (x + jy) e^{j\omega t}$$

$$V(t) = r e^{j\theta} e^{j\omega t}$$

$$\text{where } r = \sqrt{x^2 + y^2}$$

$$\theta = \arctan\left(\frac{y}{x}\right)$$

$$V(t) = r e^{j(\omega t + \theta)}$$

$$V(t) = r \cos(\omega t + \theta) + r \sin(\omega t + \theta) j$$


If we assume voltage has form $e^{j\omega t}$

then we have assumed Sines and Cosines

where the complex constant out front contains

the Amplitude of the signal and the angle.

Example

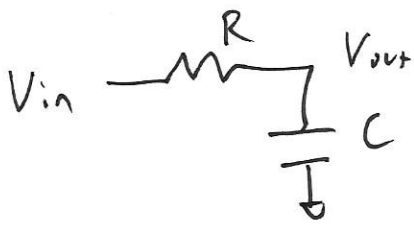

$$i = \frac{V_{in} - V_o}{R} = C \frac{dV_o}{dt}$$

$$RC \frac{dV_o}{dt} = V_{in} - V_{out}$$

Let's Assume $V_{in}(t) = 1 \cdot e^{j\omega t} = \cos \omega t + j \sin \omega t$

$$V_{out}(t) = \underbrace{F_o}_{\text{Complex \#}} e^{j\omega t} = |V_o| \cos(\omega t + \theta) + j \sin(\omega t + \theta)$$

$$-RC |V_o| \omega \sin(\omega t + \theta) + RC |V_o| \omega \cos(\omega t + \theta) j = \cos(\omega t) + j \sin(\omega t) - |V_o| \cos(\omega t + \theta) - j |V_o| \sin(\omega t + \theta)$$

Real + Imag must be zero

$$-RC\omega |V_o| \sin(\omega t + \theta) = \cos(\omega t) - |V_o| \cos(\omega t + \theta)$$

$$RC\omega |V_o| \cos(\omega t + \theta) = \sin(\omega t) - |V_o| \sin(\omega t + \theta)$$

Previously Solved "Red" Problem

Solution was

$$\tan(\theta) = -RC\omega$$

$$|V_o| = \frac{1}{\cos\theta - RC\omega \sin\theta}$$

Expand "Blue" Problem w/ trig.

$$-RC\omega|V_d| (\sin\omega t) \cos\theta + \cos\omega t \sin\theta = \cos\omega t - |V_d| (\cos\omega t \cos\theta - \sin\omega t \sin\theta)$$

Group $\sin\omega t$

$$-RC\omega|V_d| \sin\omega t \cos\theta = +|V_d| \sin\omega t \sin\theta$$

$$\tan\theta = -RC\omega \quad \text{Same as "Red" problem.}$$

Group $\cos\omega t$

$$-RC\omega|V_d| \cos\omega t \sin\theta = \cos\omega t - |V_d| \cos\omega t \cos\theta$$

$$|V_d| = \frac{1}{\cos\theta - RC\omega \sin\theta}$$

So

Solution for $\sin(\omega t)$ input
is the same as for $\cos(\omega t)$!

$$V_{in}(t) = \cos \omega t + j \sin \omega t$$

works because we solve real and imag. parts
to get a single answer.

Now, Let's use complex #s

$$V_{in} = e^{j\omega t}$$

$$V_{out}(t) = \tilde{V}_0 e^{j\omega t}$$

Complex #

$$RC \frac{d}{dt} V_0(t) = V_{in}(t) - V_0(t)$$

$$RCj\omega \tilde{V}_0 e^{j\omega t} = e^{j\omega t} - \tilde{V}_0 e^{j\omega t}$$

$$\tilde{V}_0 = \frac{1}{1 + RCj\omega}$$


Much easier than
using trig.

Recall Division is easiest in polar form

$$\vec{V}_o = \frac{1}{1 + RC\omega j} = \frac{1}{\sqrt{1 + RC^2\omega^2} e^{j\arctan(RC\omega)}}$$

$$\vec{V}_o = \underbrace{\frac{1}{\sqrt{1 + RC^2\omega^2}}}_{\substack{\text{Amplitude} \\ \text{Part of Bode plot}}} e^{-\underbrace{j\arctan(RC\omega)}_{\substack{\text{Angle, or Phase} \\ \text{of the Bode Plot.}}}}$$

Impedance

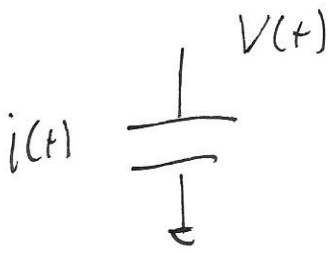

$$V(t) = \overline{V} e^{j\omega t}$$

Complex #

$$i(t) = \overline{I} e^{j\omega t}$$

Complex #

Capacitor: ~~capacitor~~

$$i(t) = C \frac{dV(t)}{dt}$$

$$\overline{I} e^{j\omega t} = C \frac{d}{dt} \overline{V} e^{j\omega t} = \boxed{j\omega C \overline{V} e^{j\omega t}}$$

\overline{I}

Define

$$\frac{V(t)}{i(t)} = \text{impedance, } Z$$

$$\frac{V(t)}{i(t)} = \frac{\overline{V} e^{j\omega t}}{\overline{I} e^{j\omega t}} = \frac{\overline{V}}{\overline{I}} = \frac{\overline{V}}{j\omega C \overline{V}} = \boxed{\frac{1}{j\omega C}}$$

Impedance of
Capacitor.

Impedance analysis

To solve circuits w/ capacitors, it is just like solving problems w/ resistors.

Now we use


$$V = I Z$$

where Z for Resistor $Z = R$
Capacitor $Z = \frac{1}{j\omega C}$


Impedance in series add:



Impedance in parallel combine too,

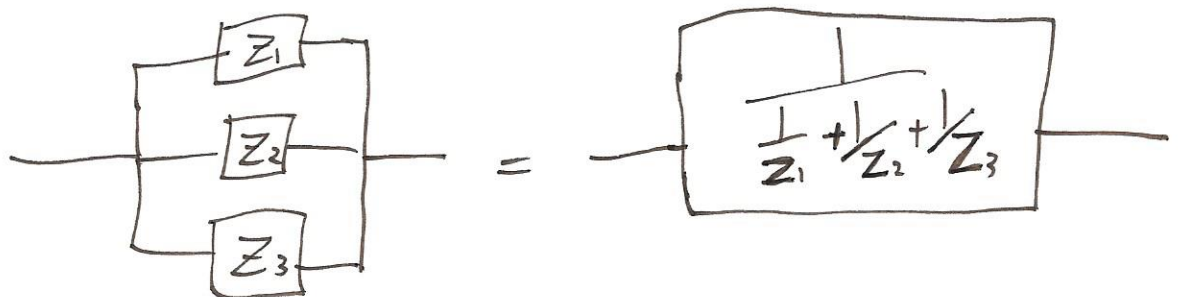

Example

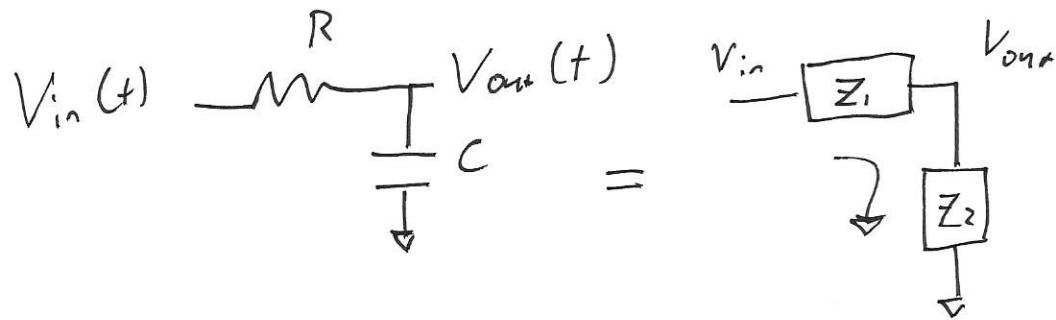

Voltage Divider


$$I = \frac{V_{in} - V_0}{Z_1} = \frac{V_{in} - 0}{Z_1 + Z_2} = \frac{V_{out}}{Z_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$\frac{V_0}{V_{in}} = \frac{1}{1 + RC\omega j}$$

Same result as before!

Let's switch the parts

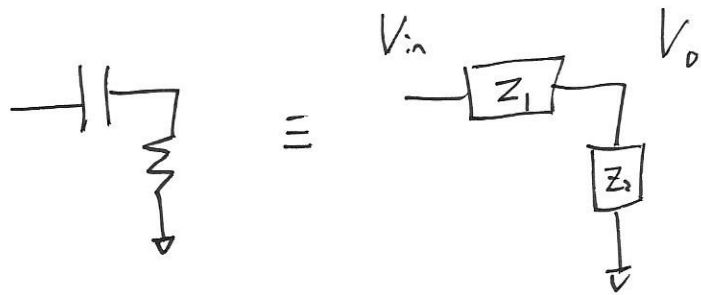

Same as last circuit

$$\frac{V_o}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$\frac{V_o}{V_{in}} = \frac{RC\omega j}{1 + RC\omega j}$$


High pass filter $RC\omega \rightarrow \infty$

$$\frac{V_o}{V_{in}} \Rightarrow 1$$

$RC\omega \rightarrow 0$

$$\frac{V_o}{V_{in}} \approx RC\omega j$$

Example w/ OP-amp

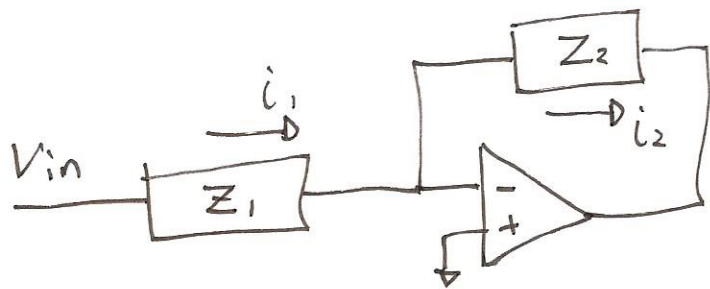


Rules for OP-amp

- $i_+ = i_- = 0$ thus $i_1 = i_2$
- $V_- = V_+ = 0$.

Thus

$$i = \frac{V_{in}}{Z_1} = \frac{-V_{out}}{Z_2} \quad \frac{V_{out}}{V_{in}} = \frac{-Z_2}{Z_1}$$

So

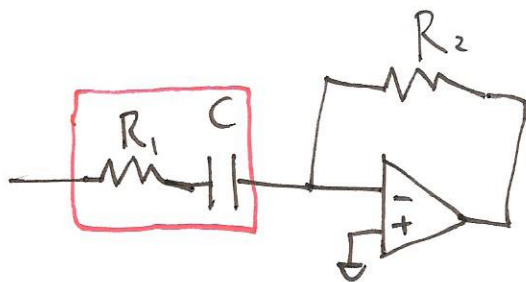

$$Z_1 = R_1 + \frac{1}{j\omega C}$$


$$Z_2 = R_2$$

$$\frac{V_{out}}{V_{in}} = \frac{-R_2}{R_1 + \frac{1}{j\omega C}} = \frac{-R_2}{R_1} \left(\frac{j\omega R_1 C}{1 + j\omega R_1 C} \right)$$

↑
Amplify

↑
High pass

Or

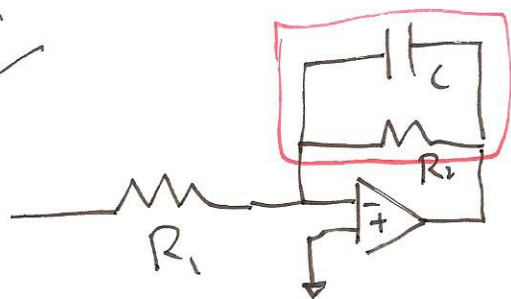


$$Z_2 = \frac{1}{\frac{1}{R_2} + \frac{1}{j\omega C}}$$

$$Z_2 = \frac{R_2}{1 + j\omega R_2 C}$$

$$\text{So } \frac{V_{out}}{V_{in}} = \frac{-Z_2}{Z_1} = \underbrace{-\frac{R_2}{R_1}}_{\text{Amplitude}} \underbrace{\frac{1}{1 + j\omega R_2 C}}_{\text{Low Pass}}$$

Or

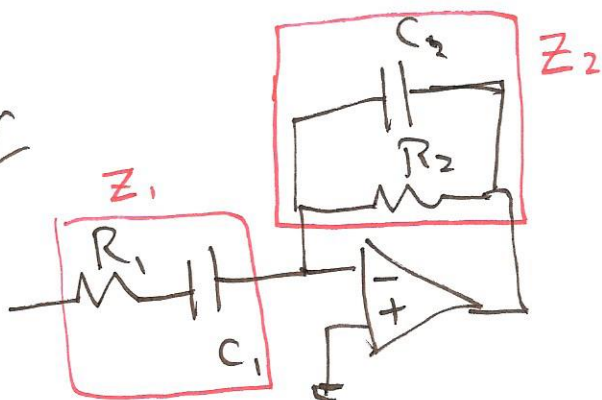

Note Z_2 , Z_1 found in prior problem 1.

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{-Z_2}{Z_1} = \frac{-R_2}{1 + j\omega R_2 C} \frac{1}{R_1 + j\omega C_1} \\ &= \underbrace{-\left(\frac{R_2}{R_1}\right)}_{\text{Amp}} \underbrace{\left(\frac{1}{1 + j\omega R_2 C}\right)}_{\text{Low Pass}} \underbrace{\left(\frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1}\right)}_{\text{High Pass}} \end{aligned}$$