


Last Week

- We represent sinusoidal, periodic signals as

$$V(t) = \underline{\underline{V}} e^{j\omega t}$$

Complex amplitude

$$j = \sqrt{-1}$$

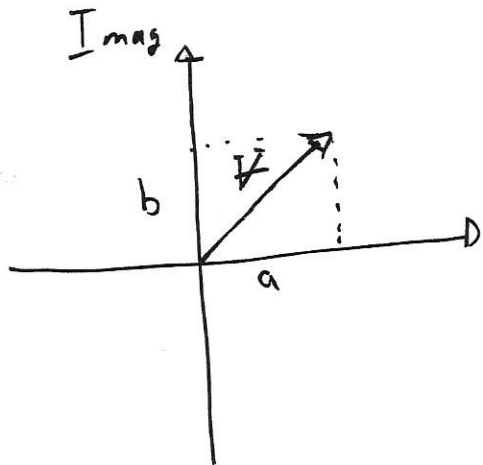

$$V = a + bj$$

$$|V| = \sqrt{a^2 + b^2}$$

$$\theta = \arctan(b/a)$$

- Complex impedance:

$$Z = \frac{V}{I}$$

where $V(t) = V e^{j\omega t}$
 $i(t) = I e^{j\omega t}$



V and I are complex amplitudes of Voltage and Current.

- Resistor $Z = R$

- Capacitor $Z = \frac{1}{j\omega C}$


- To analyze w/ impedance,

- Replace ~~at~~ all R+C w/ Z

- Analyze as though resistor.

- Substitute for Z at the end.

①

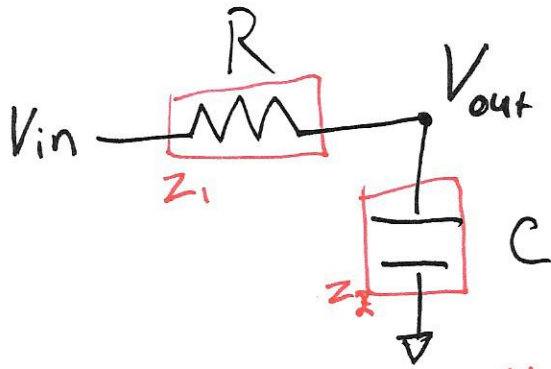


Voltage Divider

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \boxed{\frac{1}{1 + j\omega RC}}$$

②

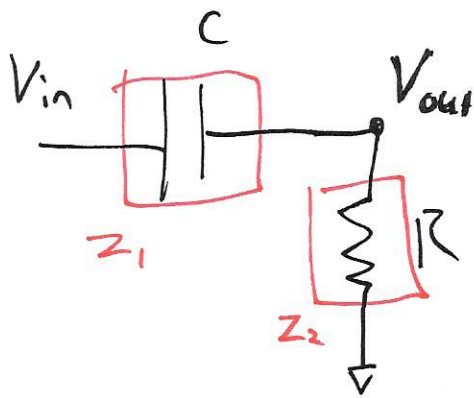

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

$$= \frac{R}{R + \frac{1}{j\omega C}} = \boxed{\frac{j\omega RC}{1 + j\omega RC}}$$

```
clear;

w = logspace(-3,3,100);
j = sqrt(-1);
RC = 1;


Vout = 1./(1+j*w*RC)
subplot(2,1,1)
loglog(w,abs(Vout))
xlabel('\omega (rad/s)'); ylabel('V_{out}')

subplot(2,1,2)
semilogx(w,angle(Vout)*180/pi)
xlabel('\omega (rad/s)'); ylabel('\theta (deg.)')

figure(1)
```

Plot example for #1


(3)

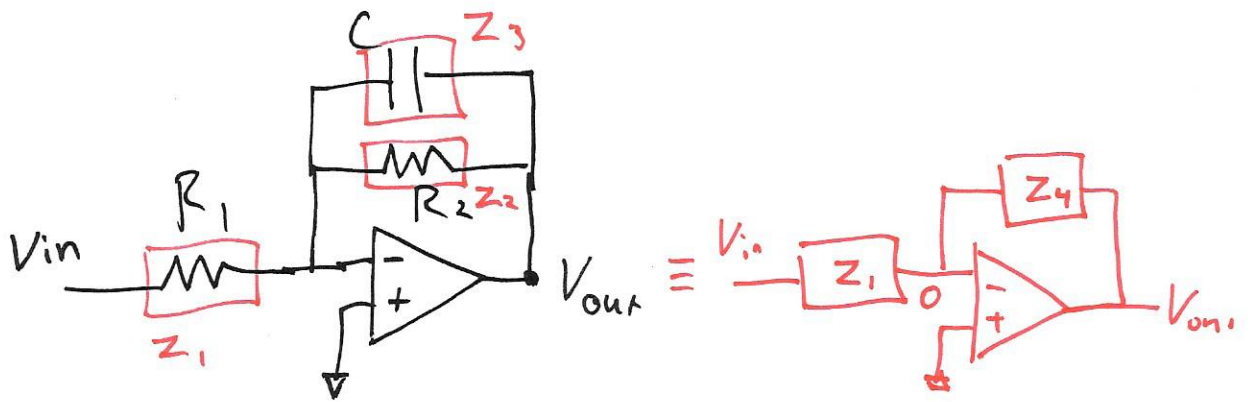

$$-V_{out} = \frac{V_{in}}{Z_1} \Rightarrow \frac{V_{out}}{V_{in}} = -\frac{Z_4}{Z_1} = -\frac{\left(\frac{1}{\frac{1}{Z_2} + \frac{1}{Z_3}}\right)}{Z_1}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\frac{1}{\frac{1}{R_2} + j\omega C}}{R_1} = \boxed{\frac{-R_2/R_1}{1 + j\omega R_2 C}}$$

(4)

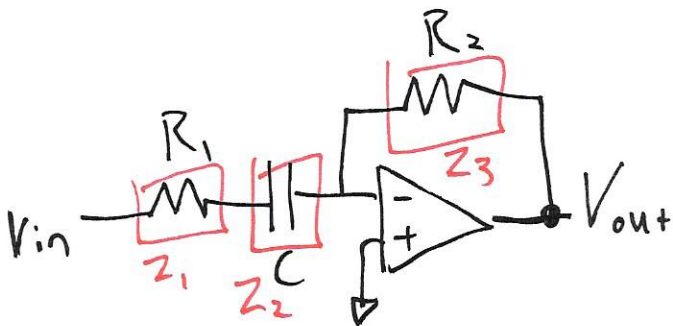


Looking at result from #3

$$\frac{V_{out}}{V_{in}} = -\frac{Z_3}{Z_1 + Z_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + \frac{1}{j\omega C}} = \frac{R_2 j\omega C}{1 + j\omega C R_1} = \boxed{\frac{\left(\frac{R_2}{R_1}\right) j\omega C R_1}{1 + j\omega C R_1}}$$

⑤

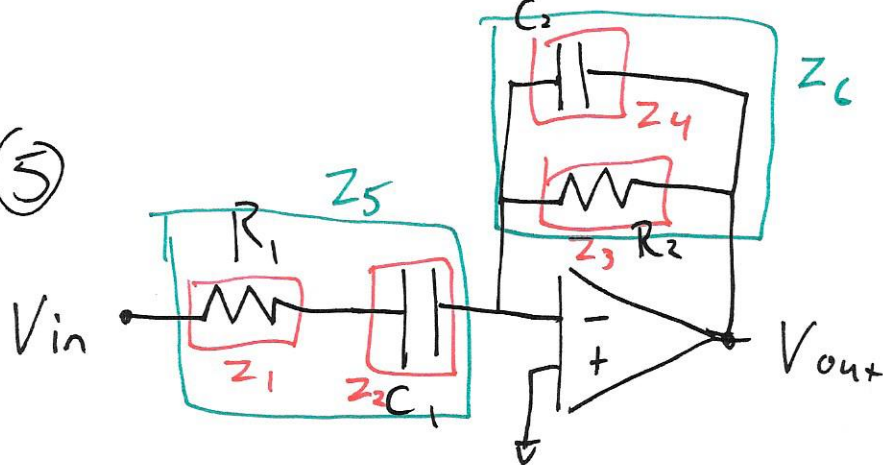



$$Z_5 = Z_1 + Z_2$$

$$Z_6 = \frac{1}{\frac{1}{Z_3} + \frac{1}{Z_4}}$$

$$\frac{V_{out}}{V_{in}} = \frac{-Z_6}{Z_5} = \frac{-\frac{1}{\frac{1}{Z_3} + \frac{1}{Z_4}}}{Z_1 + Z_2} = \frac{-1}{\frac{1}{R_2 + j\omega C_2} \cdot (R_1 + \frac{1}{j\omega C_1})}$$

$$\frac{V_{out}}{V_{in}} = \left(\frac{j\omega C_1}{1 + j\omega R_1 C_1} \right) \left(\frac{R_2}{1 + j\omega C_2 R_2} \right) = \underbrace{\left(\frac{-j\omega R_1 C_1}{1 + j\omega R_1 C_1} \right)}_{\text{High Pass}} \underbrace{\left(\frac{1}{1 + j\omega R_2 C_2} \right)}_{\text{Low Pass}} \underbrace{\left(\frac{R_2}{R_1} \right)}_{\text{Amplify!}}$$

⑥

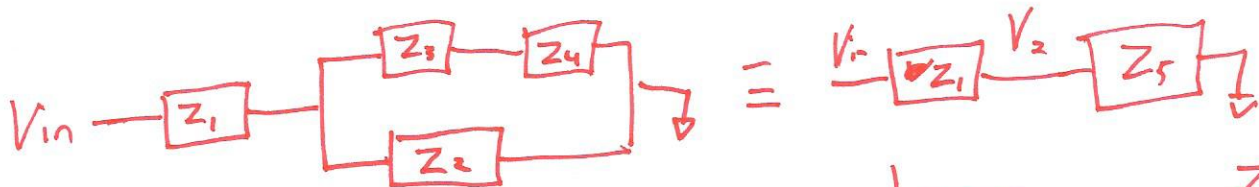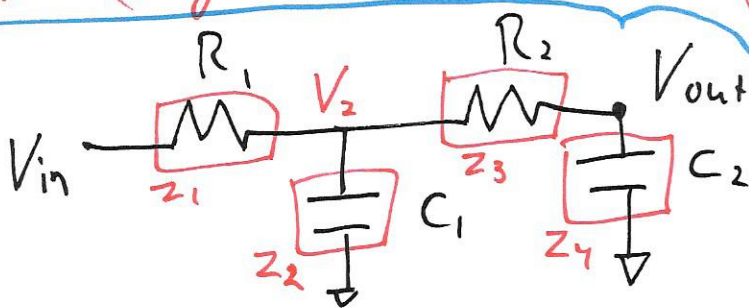

$$Z_5 = \frac{1}{\frac{1}{Z_2} + \frac{1}{Z_3 + Z_4}} = \frac{Z_2}{1 + \frac{Z_2}{Z_3 + Z_4}}$$

$$\frac{V_2}{V_{in}} = \frac{Z_5}{Z_1 + Z_5}$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_4}{Z_3 + Z_4} \cdot \frac{Z_5}{Z_1 + Z_5} \Rightarrow \text{Next Page}$$

$$\frac{V_{out}}{V_2} = \frac{Z_4}{Z_3 + Z_4}$$

$$Z_5 = \frac{Z_2}{1 + \frac{Z_2}{Z_3 + Z_4}} = \frac{\frac{1}{j\omega C_1}}{1 + \frac{\frac{1}{j\omega C_1}}{R_2 + \frac{1}{j\omega C_2}}} = \frac{1}{j\omega C_1 + \frac{1}{R_2 + \frac{1}{j\omega C_2}}}$$

$$= \frac{1}{j\omega C_1 + \frac{j\omega C_2}{1 + j\omega C_2 R_2}} = \frac{1}{j\omega C_1 \left[1 + \frac{C_2/C_1}{1 + j\omega C_2 R_2} \right]}$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_4}{Z_3 + Z_4} \cdot \frac{Z_5}{Z_1 + Z_5}$$


$$\hookrightarrow \frac{Z_4}{Z_3 + Z_4} = \frac{\frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{1}{1 + j\omega C_2 R_2}$$

$$\frac{Z_5}{Z_1 + Z_5} = \frac{\frac{1}{j\omega C_1} \cdot \frac{1}{1 + \frac{C_2/C_1}{1 + j\omega C_2 R_2}}}{R_1 + \frac{1}{j\omega C_1} \cdot \frac{1}{1 + \frac{C_2/C_1}{j\omega C_2 R_2}}} = \frac{1}{j\omega R_1 C_1 \left[1 + \frac{C_2/C_1}{1 + j\omega C_2 R_2} \right] + 1}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega C_2 R_2} \cdot \frac{1}{1 + j\omega R_1 C_1 \left(1 + \frac{C_2/C_1}{1 + j\omega C_2 R_2} \right)}$$


if $\frac{C_2}{C_1} \ll 1$
then acts
as two low
passes!

(7)

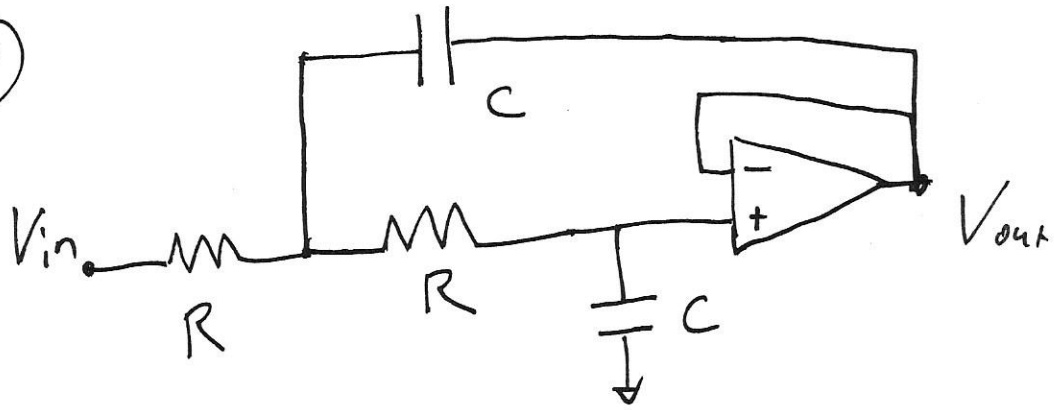

(8)

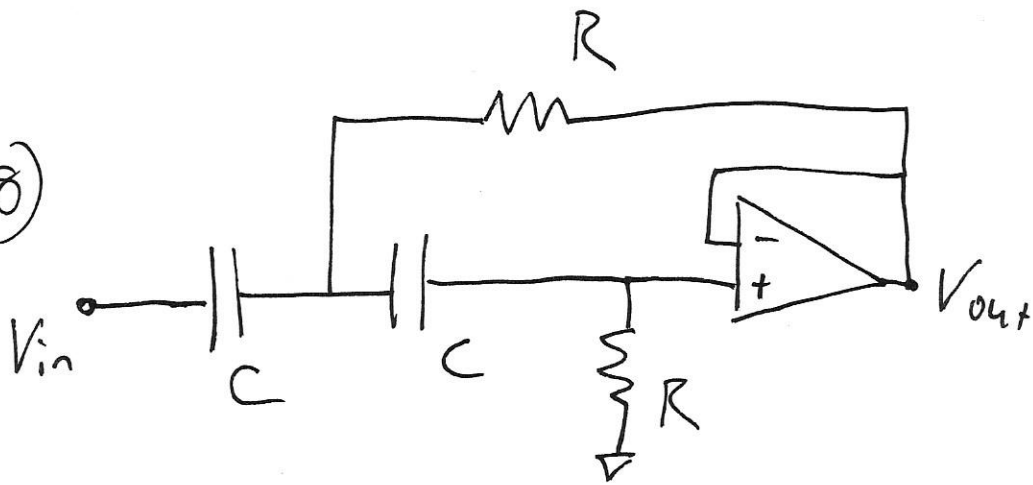

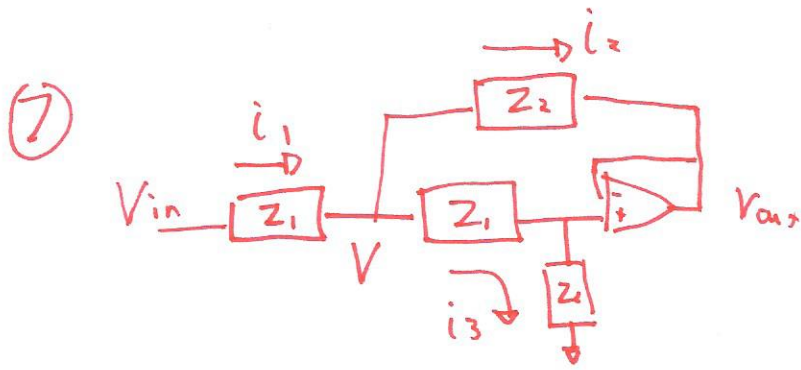

$$i_1 = \frac{V_{in} - V}{Z_1} \quad i_3 = \frac{V}{Z_1 + Z_2}$$

$$i_2 = \frac{V - V_{out}}{Z_2} \quad \frac{V_{out}}{V} = \frac{Z_2}{Z_1 + Z_2} \Rightarrow V = V_{out} \frac{(Z_1 + Z_2)}{Z_2}$$

$$i_1 = i_2 + i_3$$

$$\frac{V_{in} - V}{Z_1} = \frac{V - V_{out}}{Z_2} + \frac{V}{Z_1 + Z_2}$$

$$\frac{V_{in}}{Z_1} - V_{out} \frac{Z_1}{Z_1} \frac{(Z_1 + Z_2)}{Z_2} = V_{out} \frac{(Z_1 + Z_2)}{Z_2^2} - \frac{V_{out}}{Z_2} + \frac{V_{out} (Z_1 + Z_2)}{(Z_1 + Z_2) Z_1}$$

$$\frac{V_{in}}{Z_1} = V_{out} \left[\frac{1}{Z_2} + \frac{1}{Z_1} + \frac{1}{Z_2} \left(\frac{Z_1}{Z_2} + 1 \right) - \frac{1}{Z_2} + \frac{1}{Z_2} \right]$$

$$V_{in} = V_{out} \left(\frac{Z_1}{Z_2} + 1 + \frac{Z_1}{Z_2} \left(\frac{Z_1 + Z_2}{Z_2} \right) \right)$$

$$V_{in} = V_{out} \left(\left(\frac{Z_1 + Z_2}{Z_2} \right) \left(1 + \frac{Z_1}{Z_2} \right) \right) = V_{out} \left(\frac{Z_1 + Z_2}{Z_2} \right)^2$$

So

$$\frac{V_{out}}{V_{in}} = \left(\frac{Z_2}{Z_1 + Z_2} \right)^2$$

for #7

$$\frac{V_{out}}{V_{in}} = \left(\frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right)^2 = \left(\frac{1}{1 + j\omega RC} \right)^2 = (\text{Low Pass})^2$$

for #8

$$\frac{V_{out}}{V_{in}} = \left(\frac{R}{R + \frac{1}{j\omega C}} \right)^2 = \left(\frac{j\omega RC}{1 + j\omega RC} \right)^2 = (\text{High Pass})^2$$