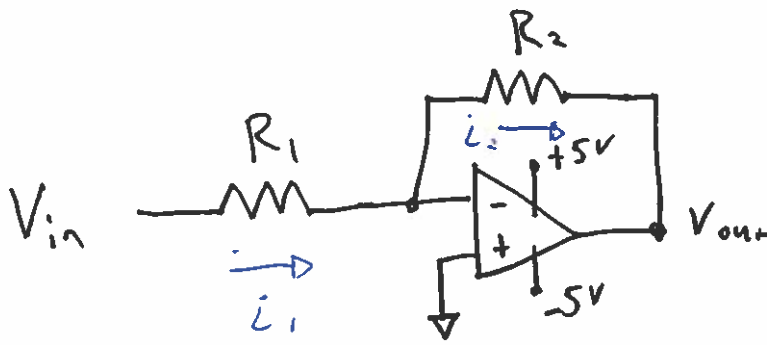



①



• $V_- = 0, i_1 = i_2$

$$\frac{V_{in}}{R_1} = i_1 = -\frac{V_o}{R_2} \Rightarrow V_o = -\frac{R_2}{R_1} V_{in}$$

②

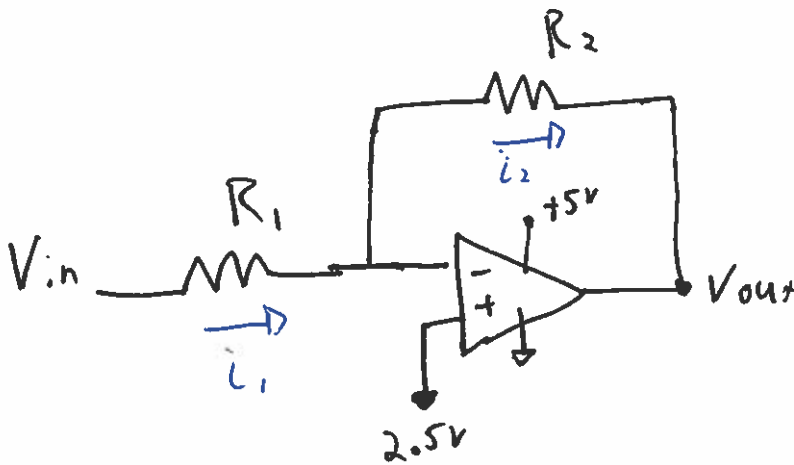

Same as above ...


• $V_+ = 2.5$

• $i_1 = i_2$

$$i = \frac{V_{in} - 2.5}{R_1} = \frac{2.5 - V_{out}}{R_2}$$

$$(V_{out} - 2.5) = -\frac{R_2}{R_1} (V_{in} - 2.5)$$

(3)

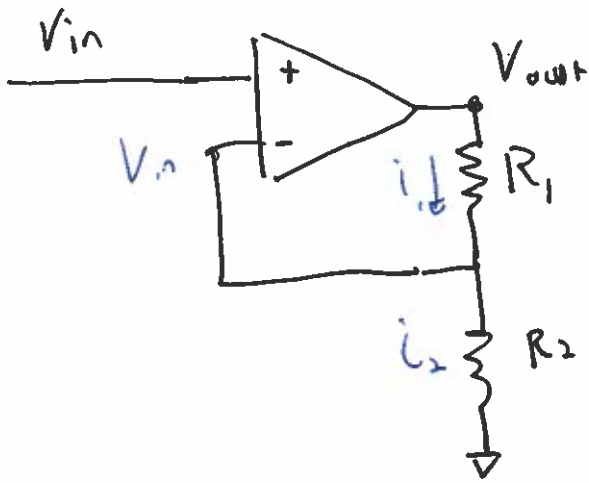


$V_- = V_{in} ; i_1 = i_2$

$i_1 = \frac{V_{out} - V_{in}}{R_1} = \frac{V_{in}}{R_2}$

$V_{out} = (1 + \frac{R_1}{R_2}) V_{in}$

(4)

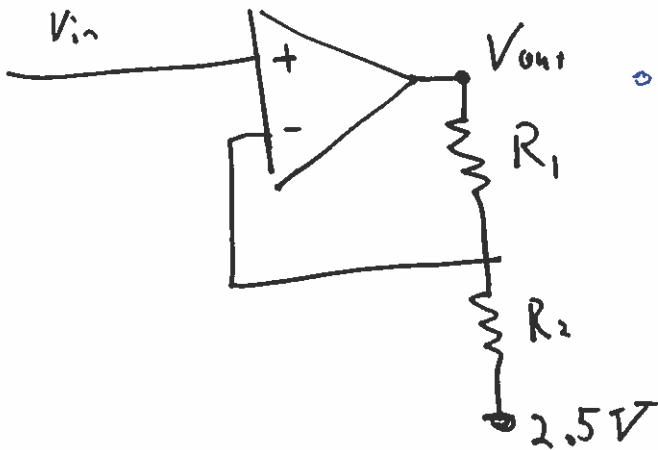

Same ...

$V_- = V_{in} ; i_1 = i_2$

$i_1 = \frac{V_{out} - V_{in}}{R_1} = \frac{V_{in} - 2.5}{R_2}$


$V_{out} = V_{in} (1 + \frac{R_1}{R_2}) - \frac{R_1}{R_2} 2.5$

-or-

$V_{out} - 2.5 = V_{in} (1 + \frac{R_1}{R_2}) - 2.5 (1 + \frac{R_1}{R_2})$

$(V_{out} - 2.5) = (V_{in} - 2.5) (1 + \frac{R_1}{R_2})$

5

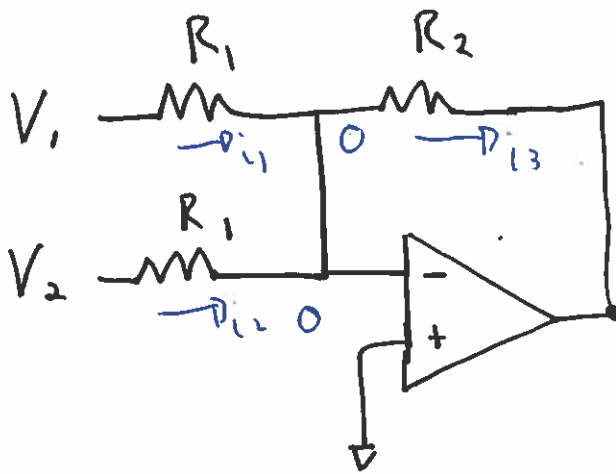


- $V_- = 0$
- $i_1 + i_2 = i_3$

$$V_{out} \quad \frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_1} = \frac{0 - V_{out}}{R_2}$$

$$V_{out} = -\frac{R_2}{R_1} (V_1 + V_2)$$

6

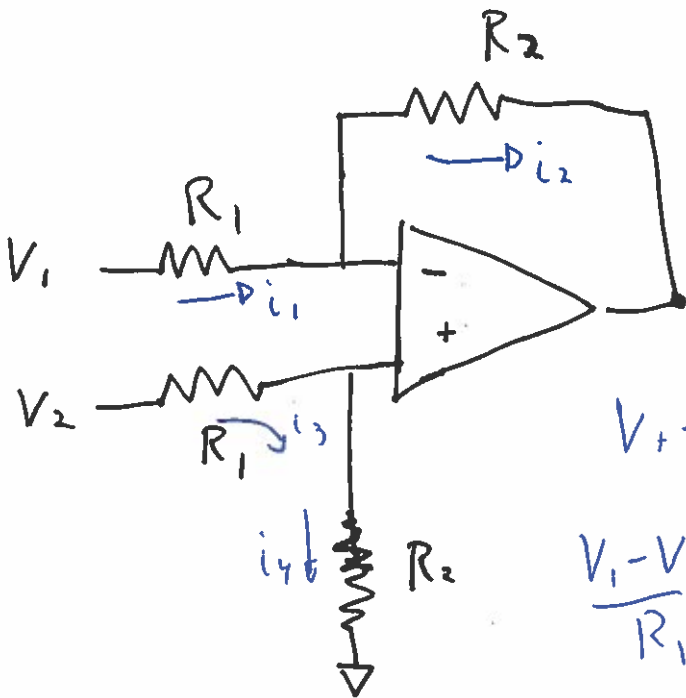

- $V_+ = V_-$
- $i_1 = i_2$ and $i_3 = i_4$

$$V_+ = V_2 \frac{R_2}{R_1 + R_2}$$

$$\frac{V_1 - V_+}{R_1} = \frac{V_+ - V_{out}}{R_2}$$

$$V_{out} = \frac{R_2}{R_1} (V_+ - V_1) + V_+$$


$$V_{out} = \frac{R_2}{R_1} \left(V_2 \frac{R_2}{R_1 + R_2} - V_1 \right) + V_2 \frac{R_2}{R_1 + R_2}$$

$$= \left(\frac{R_2}{R_1} + 1 \right) \left(\frac{R_2}{R_1 + R_2} \right) V_2 - \frac{R_2}{R_1} V_1 = \left(\frac{R_2 + R_1}{R_1} \right) \left(\frac{R_2}{R_1 + R_2} \right) V_2 - \frac{R_2}{R_1} V_1$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

(7)

See prob #6

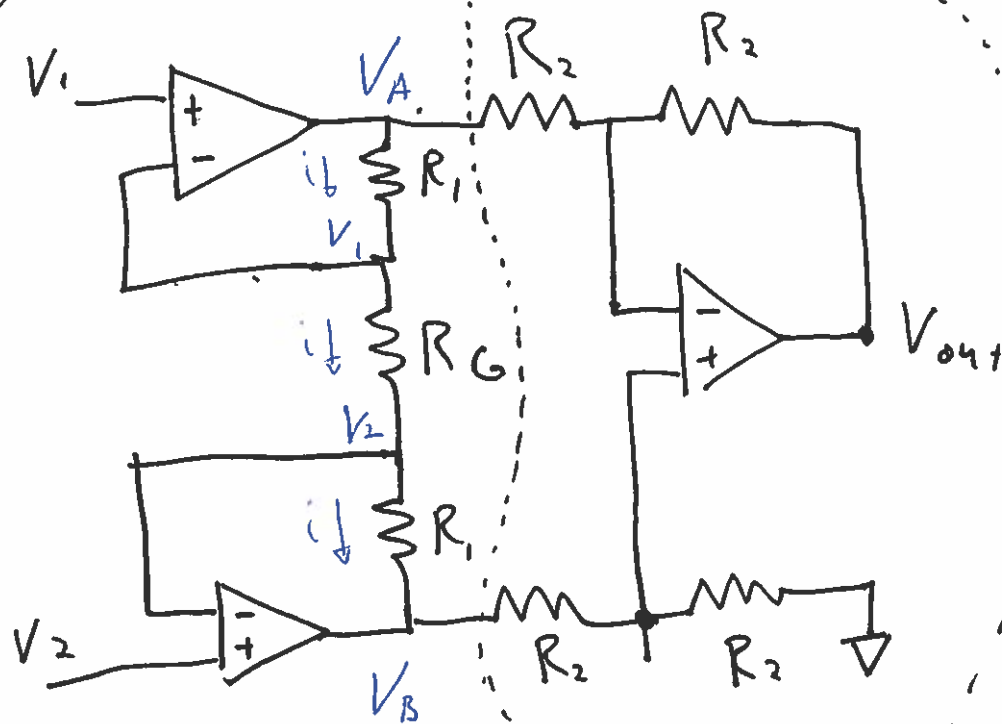

We know from #6 $V_o = (V_B - V_A)$

$$i = \frac{V_A - V_1}{R_1} = \frac{V_1 - V_2}{R_G} = \frac{V_2 - V_B}{R_1}$$


$$V_A = (1 + R_1/R_G)V_1 - V_2 \quad ; \quad V_B = (R_1/R_G + 1)V_2 - V_1$$

$$V_{out} = (V_2(1 + R_1/R_G) - V_1 - (1 + R_1/R_G)V_1 + V_2)$$

$$V_{out} = (2 + R_1/R_G)(V_2 - V_1)$$

Instrumentation Amplifier!


(8)

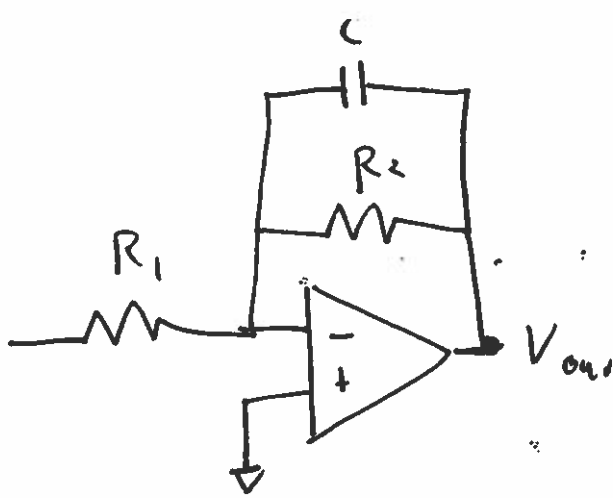

So acts like amplifier w/ gain of $-\frac{R_2}{R_1}$

Low pass filter w/ gain of $-\frac{R_2}{R_1}$ at low freq.

(9)

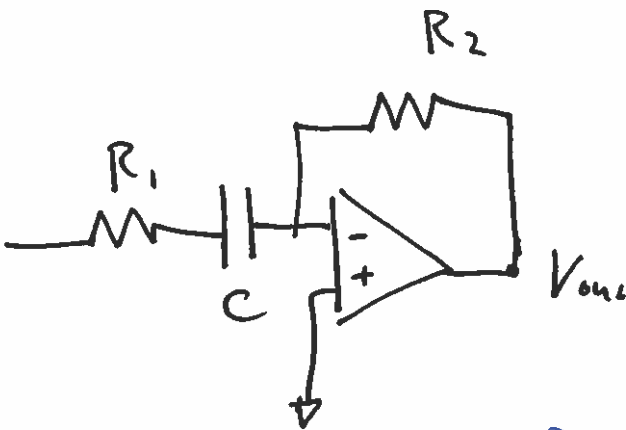

$$V_{out} = 0$$

So high pass filter w/ gain of $-\frac{R_2}{R_1}$ at high freq.