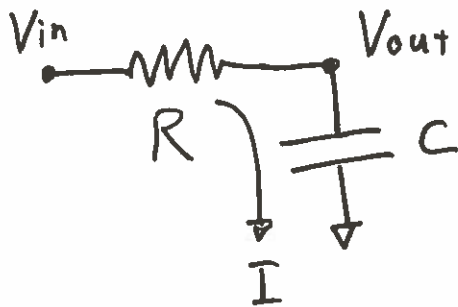


Last Week




$$\underbrace{\frac{V_{in} - V_{out}}{R}}_{\text{ohm}} = \underbrace{I}_{\text{Cap.}} = C \frac{dV_{out}}{dt}$$

$$RC \frac{dV_{out}}{dt} = (V_{in} - V_{out})$$

Sq. Wave \Rightarrow Solution is of the form

$$e^{-t/RC}$$

Your Task

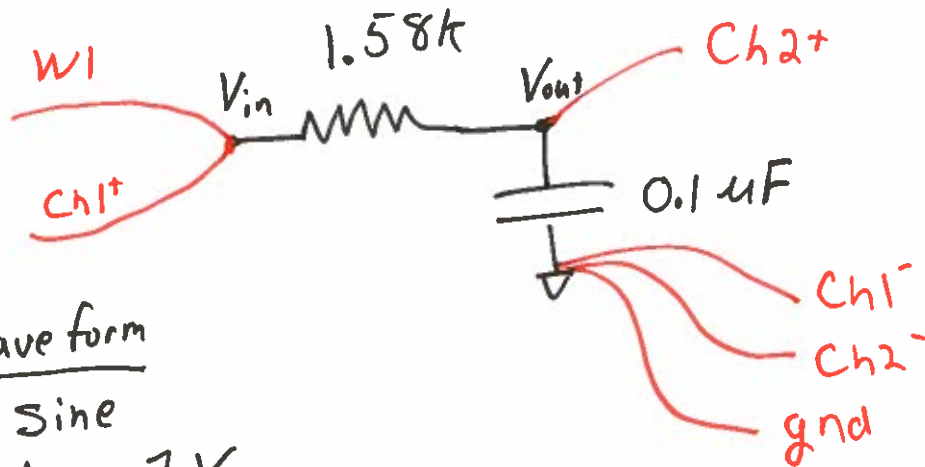


Wave form

Sine
Amp = 1V
offset = 0V
Vary freq.




Questions

- How does the freq. of V_{out} change as you adjust the freq. of V_{in} ?
- How does amplitude of V_{out} change as you adjust the freq. of V_{in} ?
- How does the phase of V_{out} relative to V_{in} change as you adjust freq. of V_{in} ?
- Why did I use 1.58k?
- Any other observations?


Linear Systems

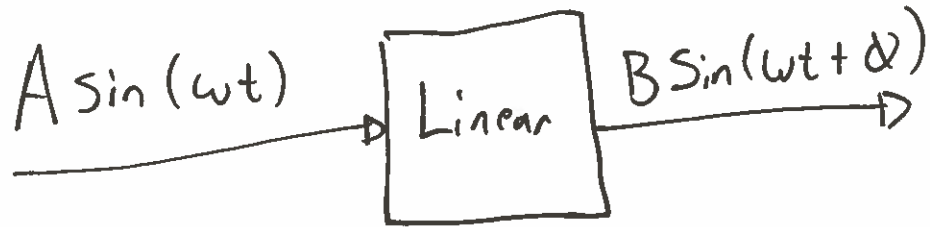

Example

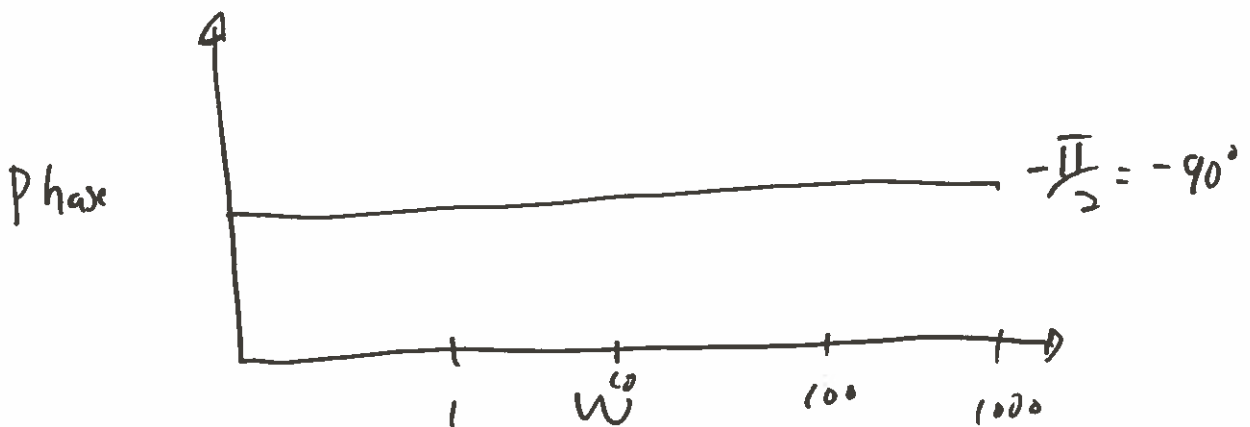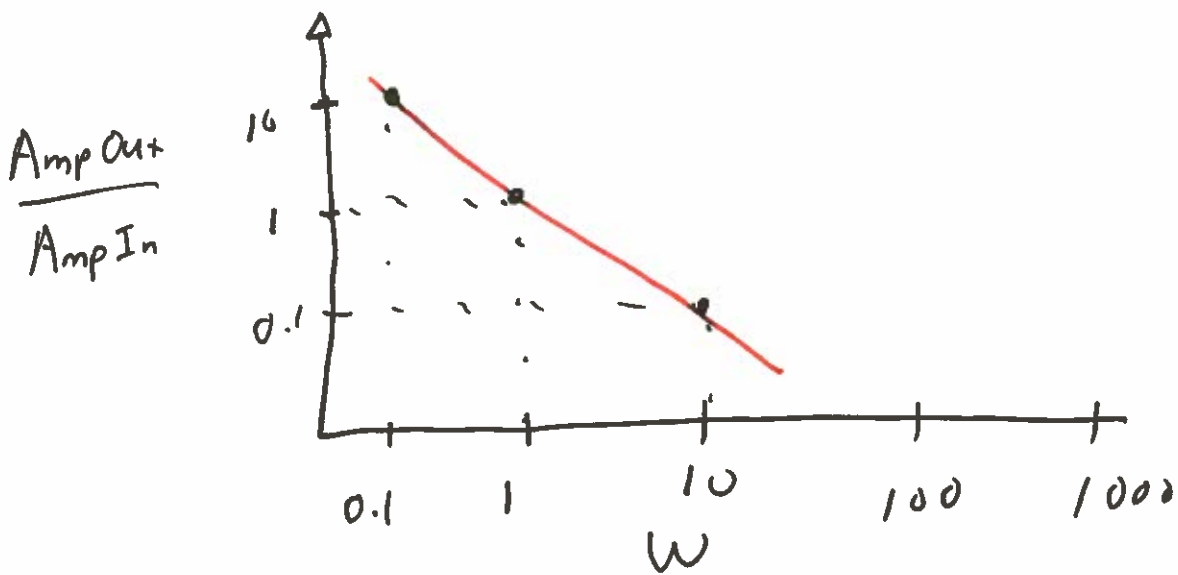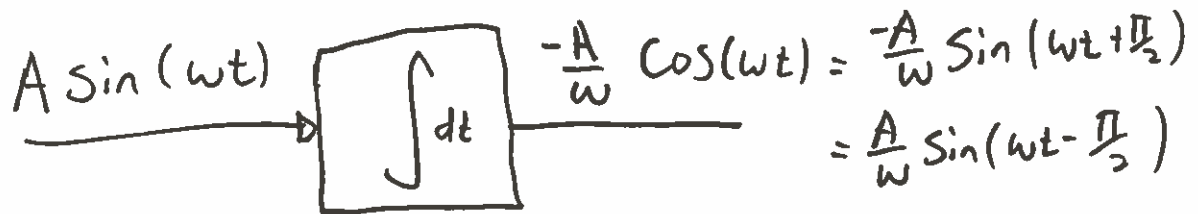

Analysis

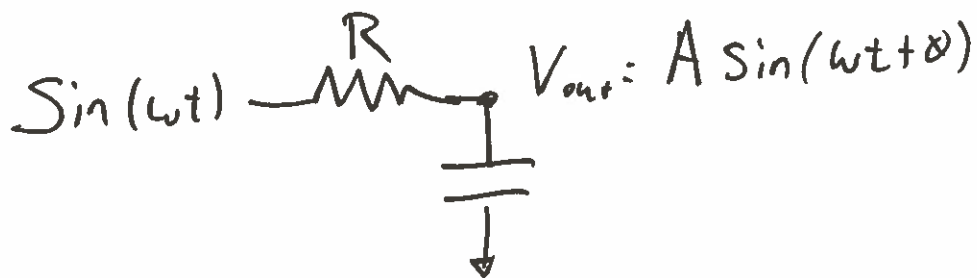

$$RC \frac{dV_o}{dt} = -(V_{in} - V_{out})$$



See notes but notice that
D.E. turns to a trig. eqn.

Final Result

$$\phi = \text{atan}(-RC\omega)$$


$$A = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$

ω is in rad/sec

Experimentally

Check these formula at a few data points

Sketch

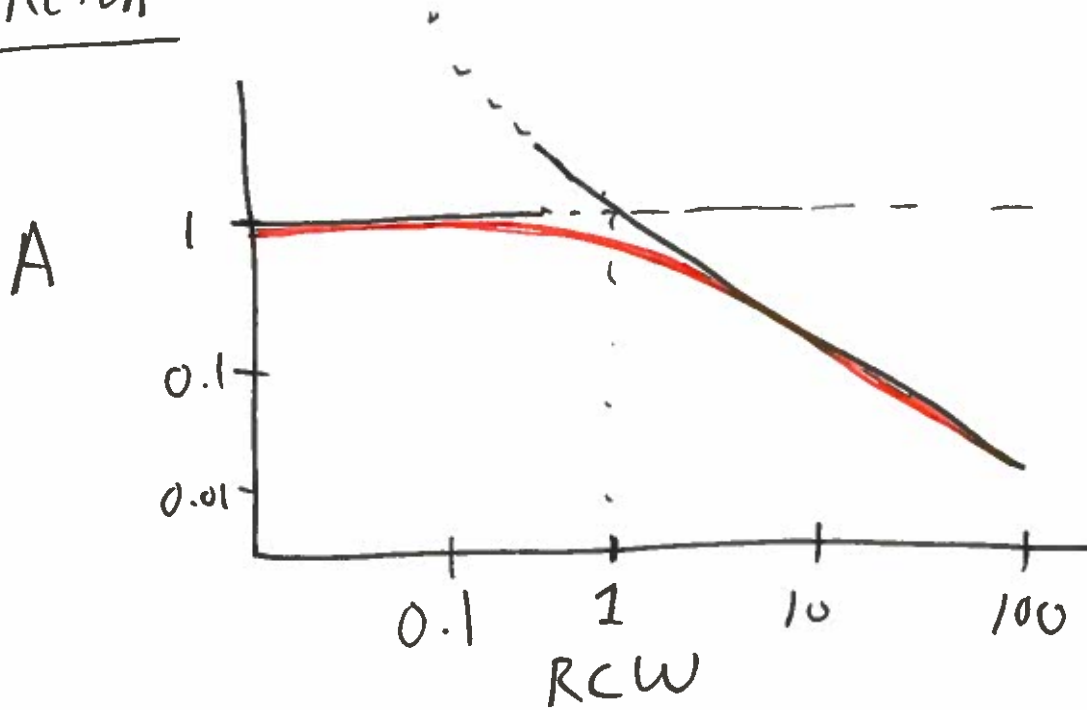

- Show Bode plot tool in wave forms.
- Demo changes in R and C.