
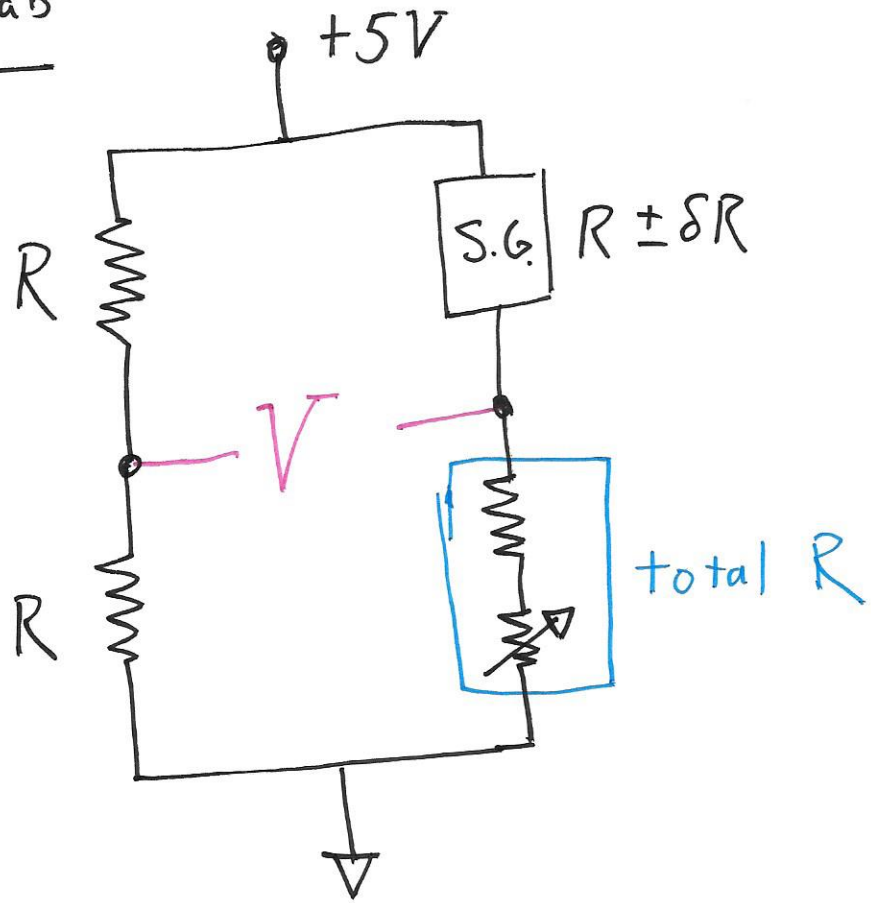


Review Lab

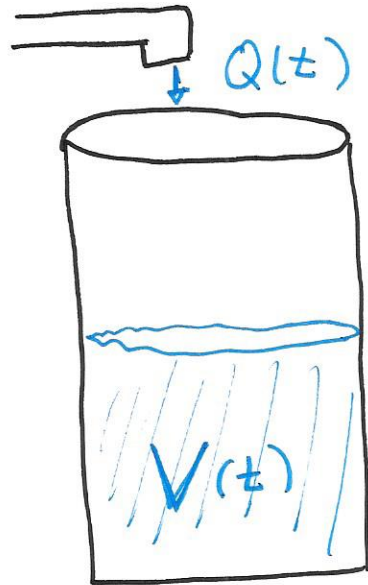

Tank



$$V(t) = V(t=0) + \int Q dt$$


Since Height is like Voltage

$$A(H - H(t=0)) = \int Q dt$$

-OR-

$$A \frac{dH}{dt} = Q$$

Capacitor

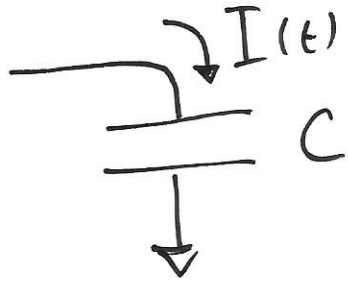



$$C(V - V(t=0)) = \int I(t)$$

- or -

$$C \frac{dV}{dt} = I$$

Let's prove it experimentally



#1

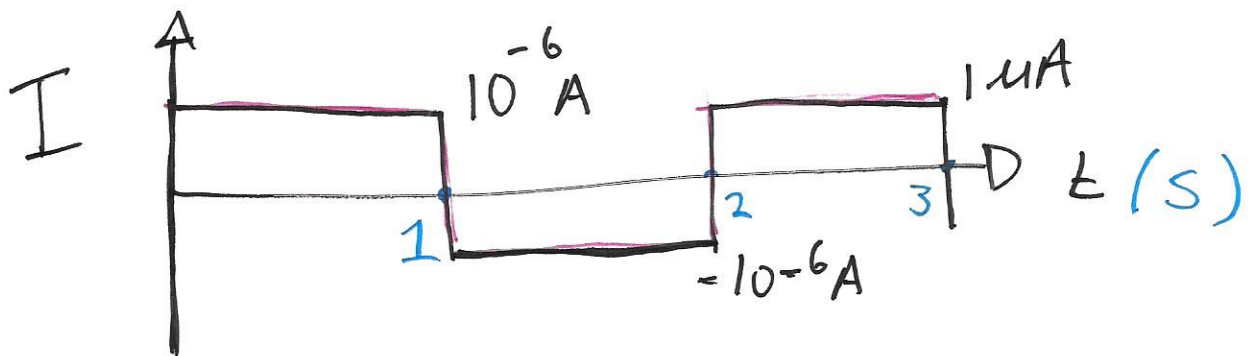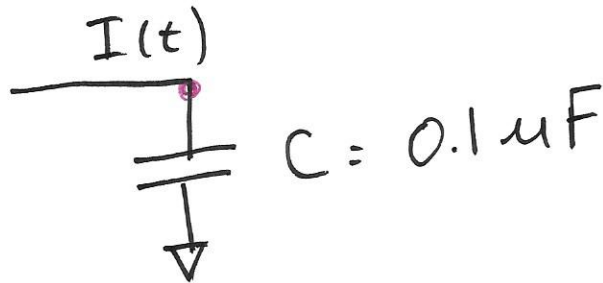

Sketch $V(t)$ (Voltage across Capacitor)

WITH UNITS!



#2

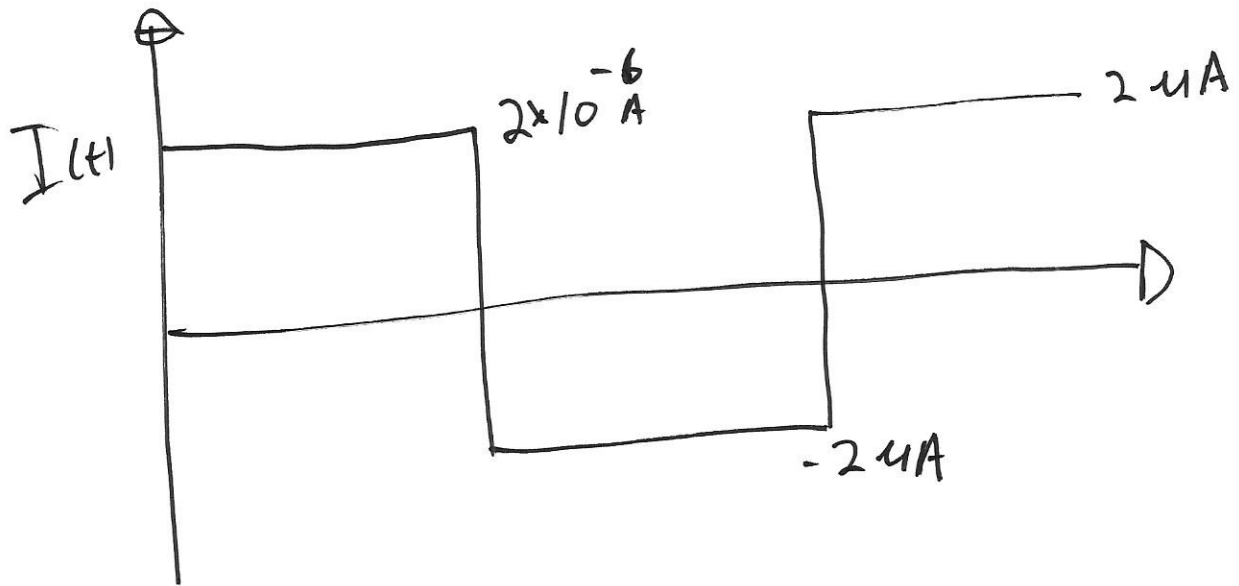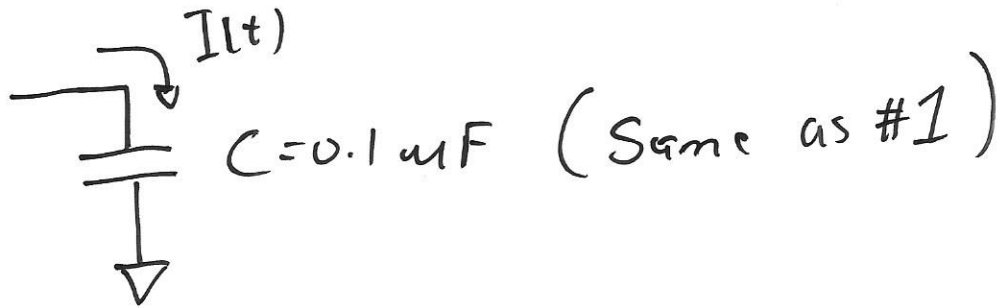

Double I from #1

Sketch $V(t)$



#3

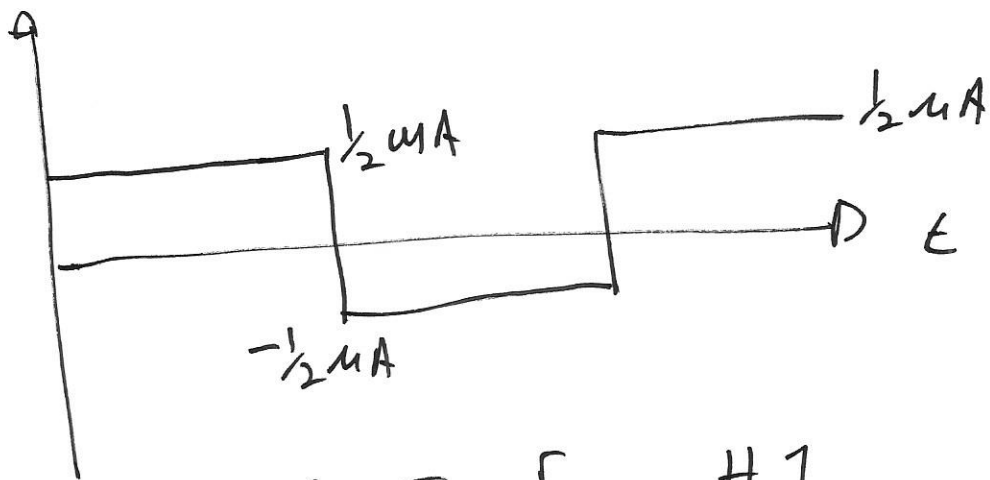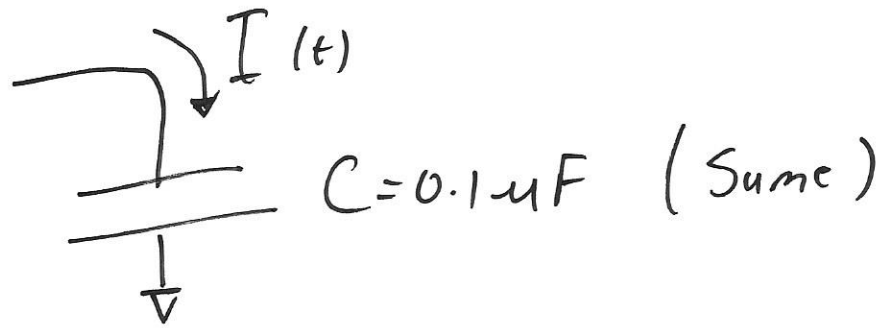

Half I from #1

Sketch $V(t)$



#4

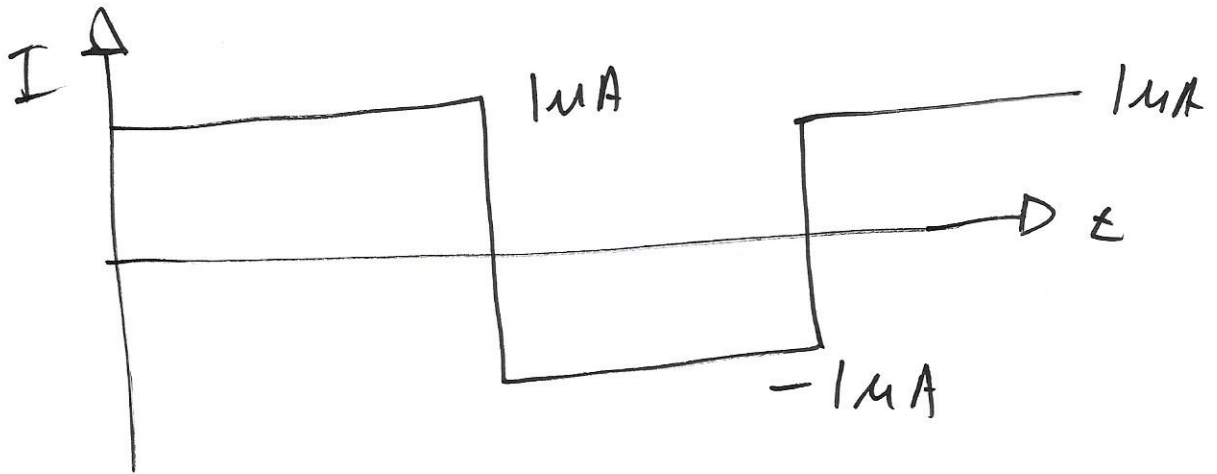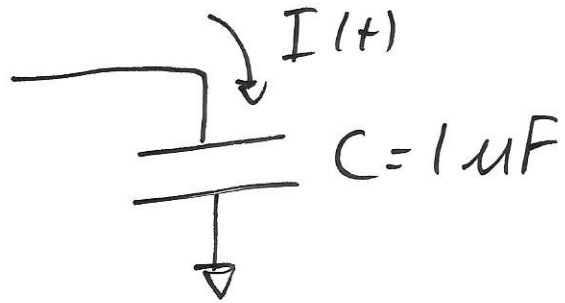

$C = 1 \mu F$ $10 \times$ #1


Sketch $V(t)$

#5

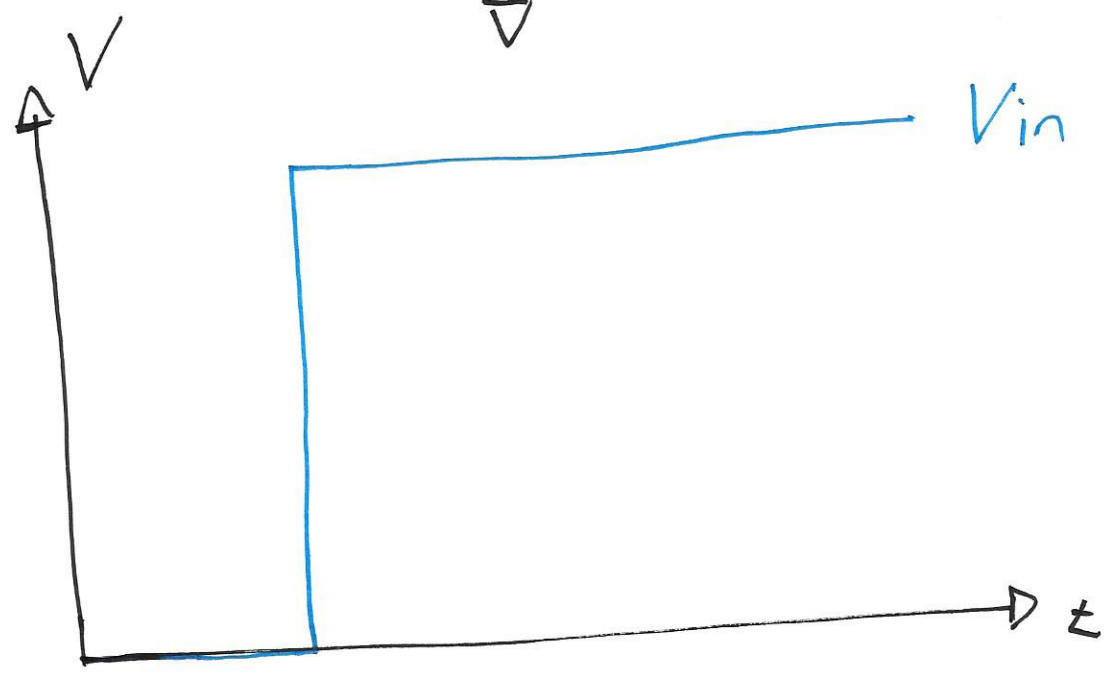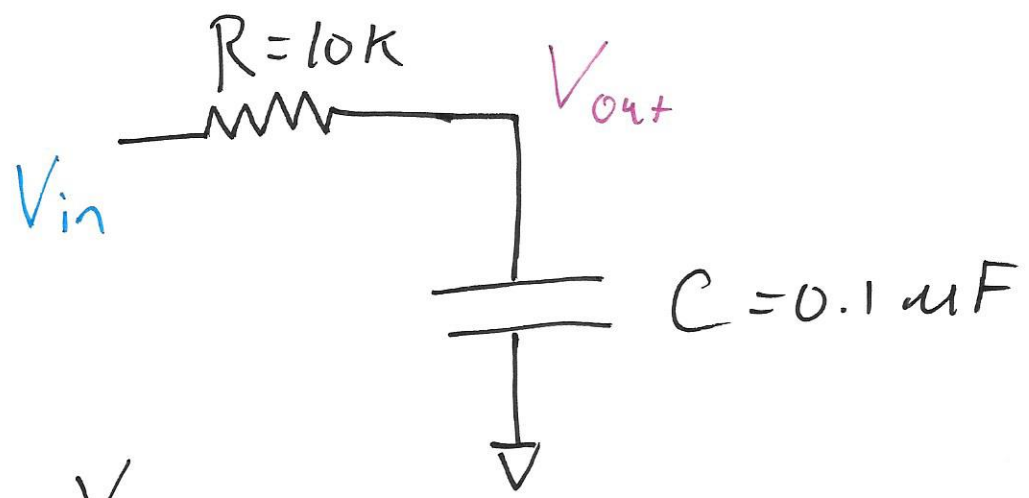

Sketch V_{out}
With Units

#6

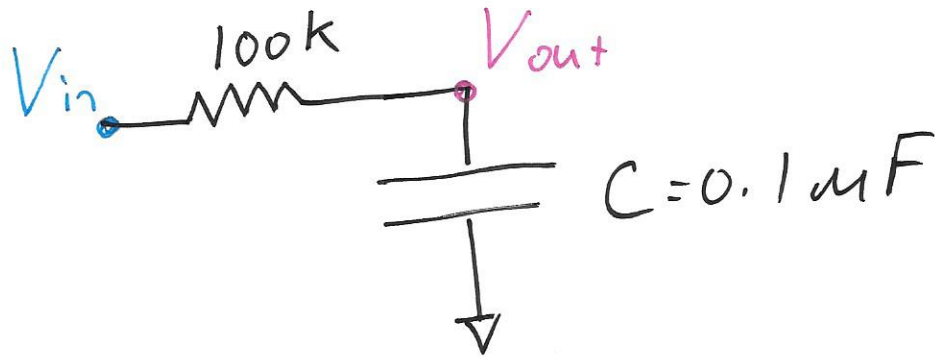

Sketch V_{out} for same V_{in}
as previous - on SAME plot