

Lab: Set current, measure voltage

A useful circuit for exploring the relationship between voltage and current is shown in Figure 4. Here “Black Box” means I can place any analog component there. By controlling the input voltage and selecting an appropriate value of the resistor, I can control the current flowing through the “Black Box”. By measuring the output voltage of the lower op-amp, I can measure the resulting voltage **across** the Black Box.

First, try to understand this general circuit using our rules when op-amps are wired in negative feedback

- No current flows into the op-amp’s inputs.
- The input voltages are equal.

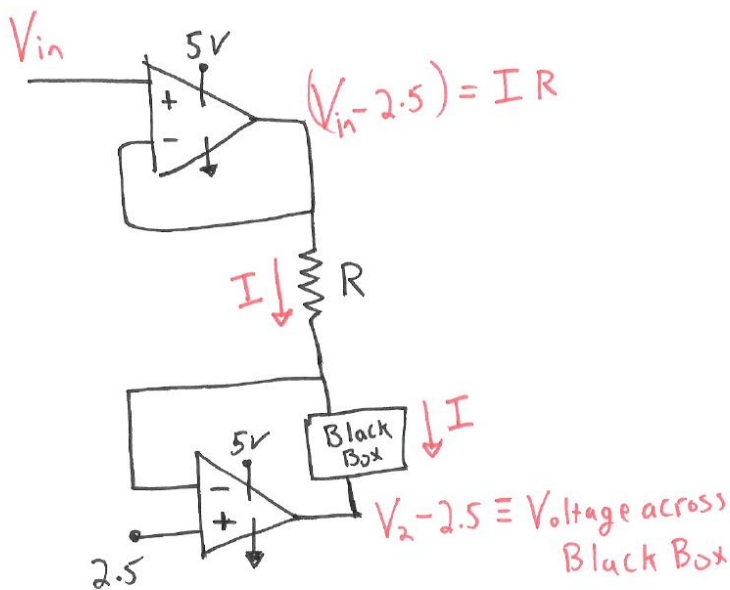


Figure 1: Generic source current, measure voltage circuit.

Now let’s test the voltage and current relationship for two devices. First, is the capacitor. Build the circuit shown Figure 5a. For the components:

- Your “Black box” should be a 0.1 μF capacitor.
- Your resistor should be 1 M
- Your input voltage should be 1 V amplitude, 2.5 V offset, 0.5 Hz **square wave**.
- Measure the output of op-amp 1 with Ch1+ and output of op-amp 2 with Ch 2 +. Place Ch1- and Ch2- into 2.5 V.

For each step change in V_{in} (the current through the capacitor) you should observe that the voltage across the capacitor changes linearly, until the system saturates. Using the scope's cursor measure dV/dt for the voltage across the capacitor. Change the input amplitude to 5 different values (therefore changing the current through the capacitor) and measure dV/dt across the capacitor. **Note the max value the waven can output when plugged into only the computers USB is 5V – therefore do not make the amplitude greater than 2.5V.** Make a table that provides your different values of current, your measured dV/dt , and therefore the measured value of the capacitance. Did you verify our basic capacitor law, $\frac{dV}{dt} = I$?

Second black box to test, is a light emitting diode, LED. Build the circuit shown Figure 5b. For the components:

- Your “Black box” should be a red LED.
- Your resistor should be 100 Ohms
- Your input voltage should be 1 V amplitude, 2.5 V offset, 10 Hz **SINE wave**.
- Measure the output of op-amp 1 with Ch1+ and output of op-amp 2 with Ch 2 +. Place Ch1- and Ch2- into 2.5 V.
- On the scope, add an x-y plot. Look up what a V-I curve for an LED is and check that your x-y plot makes sense to you.

Save the data for Channel 1 and Channel 2. In your lab report you will want to make a plot where voltage across the LED is on the x-axis and current through the LED is on the y-axis. Note that you are measuring only voltage, but you can infer the current since you know that the circuit has a 100 ohm resistor.

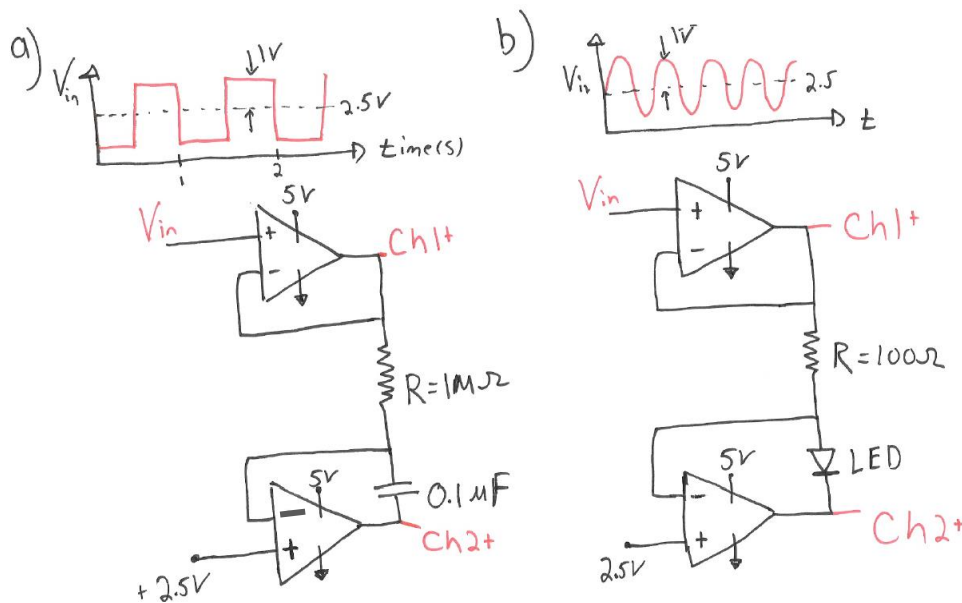


Figure 2: Check the V-I behavior of a capacitor and a LED.