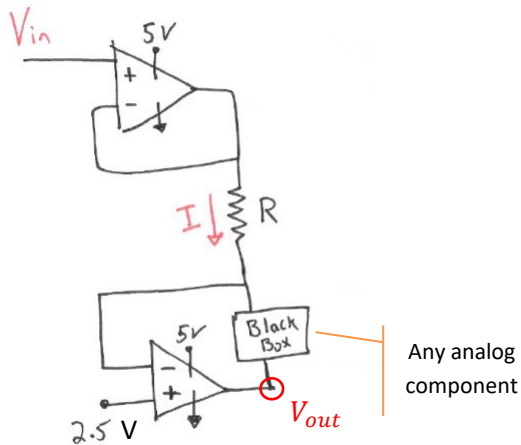


## Lab: Controlling Current with Op-Amps

**Goals:** 1. Use negative feedback of an op-amp to control current; 2. Verify the theoretical  $V - I$  characteristics of a capacitor and a light-emitting diode using a controlled current.

### Warm up: Op-Amps in negative feedback

A useful circuit for exploring the relationship between voltage and current is shown in Figure 1.



*Draw a boundary around any op-amp to the left that is wired in "negative feedback."*

Figure 1: Generic source current, measure voltage circuit.

First, let's try to understand this general circuit using our rules when op-amps are wired in **negative feedback**:

- $I_{in}^+ = I_{in}^- \approx 0$
- $V_{in}^+ = V_{in}^-$




*Applying  $V_{in}^+ = V_{in}^-$ , determine the voltages at the following colored nodes?*



*Write the values on the circuit schematic.*



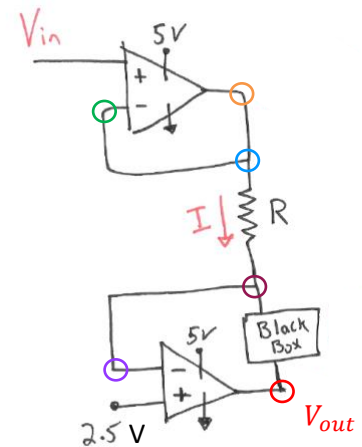*Applying  $I_{in}^+ = I_{in}^- \approx 0$ , write an equation for  $I$  and for  $I_{BlackBox}$*



By controlling  $V_{in}^+$  and selecting an appropriate value of  $R$ , I can control  $I_{BlackBox}$ .



How can you determine the voltage dropped across the Black Box?

### Part I: Verifying the I-V behavior of a capacitor

- Build the circuit shown Figure 2a) using the [LMC6484A](#) chip which has the pin configuration pictured in Figure 2b) . (You might want to redraw 2a) using 2b) before you build it.)

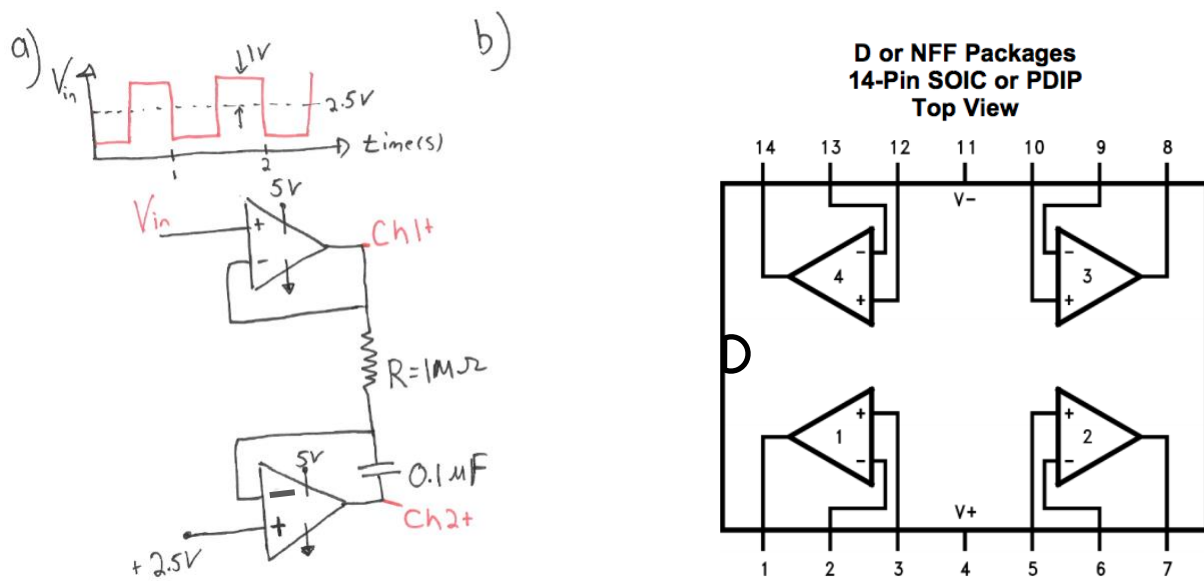


Figure 2. a) Circuit to test the capacitor performance, b) Pin configuration of LMC6484A chip.



$V^-$  and  $V^+$  are source or “rail” voltages that supply all the op-amps.

$$V^- = V_s^-, V^+ = V_s^+$$

$$V_s^- =$$

$$V_s^+ =$$

- Connect the Analog Discovery to the circuit; Set Wavegen using the  $V_{in}$  signal of Figure 2a).

**Ensure the Discovery GROUND and the op-amp GROUND ( $V_s^-$ ) are equal.**




Use Wavegen 1 as the  $V_{in}^+$   
Use Scope Channels 1 & 2 as shown;  
Your reference voltage is +2.5V.



Where do you connect  $Ch1^-$  and  $Ch2^-$ ?

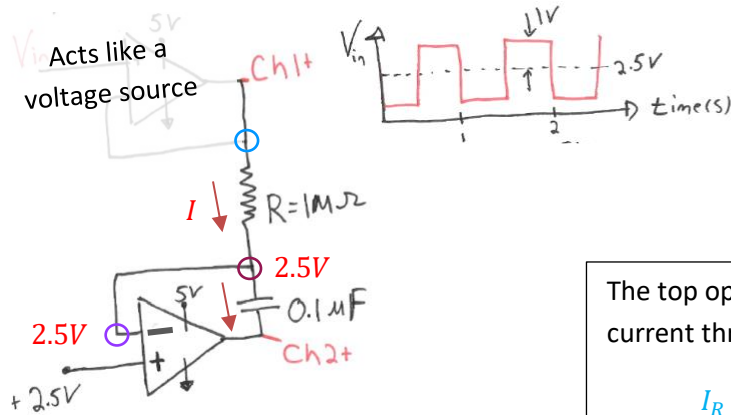3. Assess the expected voltage across the capacitor:



The top op-amp forces a current through the capacitor:

$$I_R = I_{cap} = ?$$



You can think of current as charged particles flowing in time, in fact, 1 Amp = 1 Coulomb of charge /second.

What does the capacitor do with the charge flow?

To see if you're getting the output that you expect, we'll have to recall that


$$I_{capacitor} = c \cdot \frac{dV}{dt},$$

where  $c$  is the capacitance of the capacitor and  $\frac{dV}{dt}$  is the change in voltage across the capacitor with time.

Let's rearrange this equation and integrate:

$$\frac{1}{c} \int I_{capacitor} dt = \int dV$$

We're only looking at 1/2 a cycle

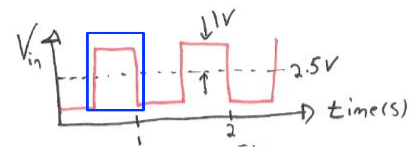

And since the voltage is constant during the 1/2 cycle that we are integrating over,

$$\frac{1}{c} \int \frac{V_{in} - 2.5}{R} dt = V(t)$$

$$\frac{1}{cR} t = V(t)$$



What should  $V(t)$  v.  $t$  look like over the whole period?

Is your capacitor functioning as expected?


4. Let's verify the theoretical behavior of a capacitor,  $\frac{dV}{dt} = \frac{1}{C} \cdot I_{capacitor}$

Using Wavegen, change  $V_{in}$  (therefore changing  $I_{capacitor}$ ). Use 5 different  $V_{in}$  (*all*  $> 0 V$ ) and measure  $\frac{dV}{dt}$  across the capacitor. Fill in the table below.



*In choosing my range of  $V_{in}$  values, what is my  $V_{max}$ ?*

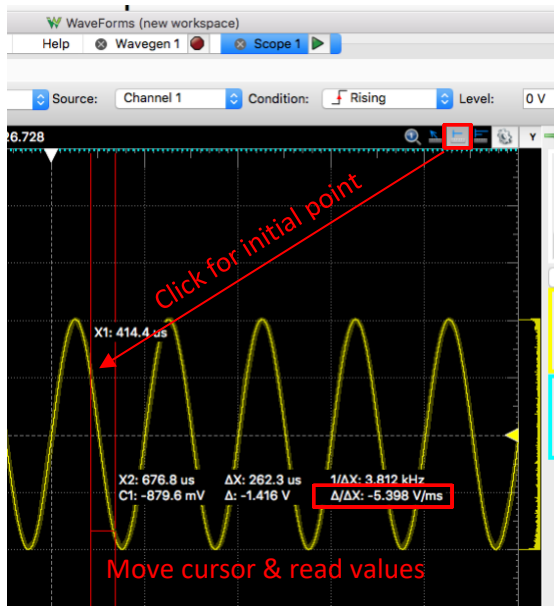To measure  $\frac{dV}{dt}$ , use the **vertical** cursor tool on your dataset (*data shown is fake*):



$V_{in}$ (Volts)	$\frac{dV}{dt}$ (measured) Volts/second





Did you verify our basic capacitor law,  $\frac{dV}{dt} = \frac{1}{C} I$  ?

**Save to turn in.**

## Part I: Verifying the $I$ - $V$ behavior of a light-emitting diode

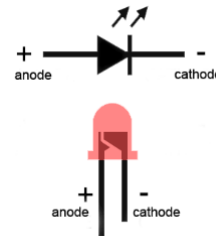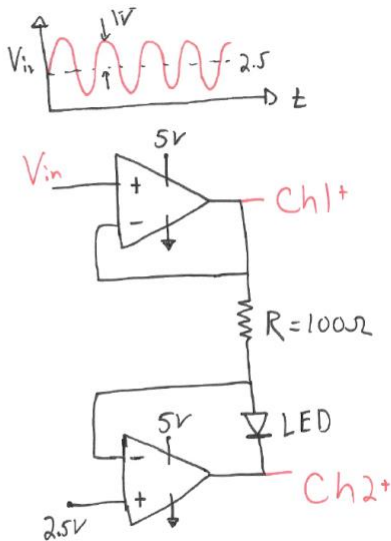5. The second Black Box to test is a light emitting diode, LED. Build the circuit shown Figure 3.



<https://www.allaboutcircuits.com/tools/led-resistor-calculator/>

Figure 3. Circuit using LED as Black Box.

6. Connect the Analog Discovery and adjust the settings on Waven to  $V_{in}$  in Figure 3.



Ensure the Discovery GROUND and the op-amp GROUND ( $V_s^-$ ) are equal.

Use Waven 1 as the  $V_{in}^+$   
Use Scope Channels 1 & 2 as shown;  
Your reference voltage is +2.5V.



Where do you connect  
Ch1<sup>-</sup> and Ch2<sup>-</sup>?

7. On the scope, add an x-y plot. An idealized V-I curve for an LED looks something like [this](#)



Which of Ch1 or Ch2 represents  $I$  (y-axis)?

Check to see that your x-y plot makes sense.

Save the data for Channel 1 and Channel 2. In your lab report you will want to make a plot where voltage across the LED is on the x-axis and current through the LED is on the y-axis. Note that you are measuring only voltage, but you can infer the current since you know that the circuit has a 100 ohm resistor.

