

Lab assignment: Using Capacitors to Measure Humidity


Goal: Sense and compute relative humidity by measuring capacitance.

How can we sense humidity with a capacitor?

Now that you've been in Needham, Massachusetts for a few weeks, you've experienced humidity!

%RH *Relative humidity* is the percent of water vapor in the air *relative* to how much water vapor the air can hold before the water condenses—that is, before it rains or snows, depending on the temperature.

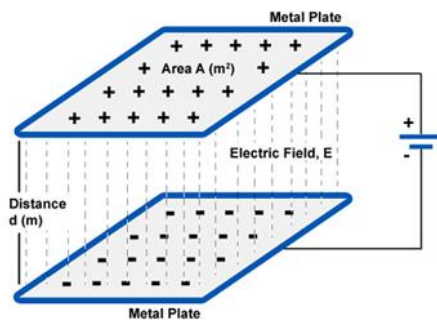A capacitor is something that has the “capacity” to store charge. Often the charge is stored across parallel plates of metal, like so:



We normally refer to separated + and - charges as “electric potential differences” or “Voltage differences.”


$$\text{Capacitance} = \frac{\text{charge stored}}{\Delta V}$$

It turns out that we can increase the charge stored in a parallel-plate capacitor by placing a non-conducting material between the plates.

Source: <https://sites.google.com/site/nithinjoseph2066/electromagnetics/parallel-plate-capacitor>

In the case of this lab, for the humidity sensor, the material between the capacitor plates is a water-sensitive polymeric (i.e., plastic) material, likely cellulose ester.

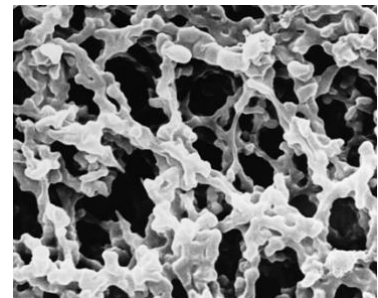It's made from sugar molecules and looks like this in an electron microscope: The cellulose ester scaffolding is about 10,000 times smaller than the thickness of a human hair.




Source: <https://www.labsupply.co.nz/>


Water vapor from the air attaches to the surface of the cellulose ester fibers, enabling more charge to be stored in the capacitor:

Capacitance ↑ with ↑ %RH

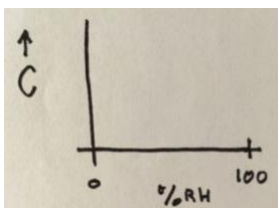You are going to create a circuit that uses this [humidity sensor](#) as the *transducer*. Roughly, what does the *transfer* or *reference* curve for your sensor look like?



Hint: Manufacturers publish performance data on the sensors they sell. They want you to know exactly how it will perform in a circuit and under what *circuit conditions* it will perform this way.

transducer: a device that converts one physical quantity to another e.g. 

Under what *circuit conditions* (Hz, voltage input) was this *reference* curve generated?

Part 1. Calibrating a circuit for your %RH sensor


Goal: Create a circuit that you can use to measure %RH with this [humidity sensor](#) transducer.

You'll *calibrate* this circuit by simulating the circuit test conditions of the manufacturer. You'll use capacitors of known values in the range of the transducer's response: 160 to 190 pF. You will record the circuit's response in Root Mean Square (RMS) Voltage. [Look up the difference](#) between different types of amplitude---dialogue with a neighbor, ninja or instructor about this question:

How is the V-RMS different from the V-peak and V-peak-peak? (Can you sketch a graph that illustrates?)

After you develop your calibration curve, you'll substitute the [humidity sensor](#) for the [capacitor](#) in the circuit (Part 2).

1. Build the circuit shown

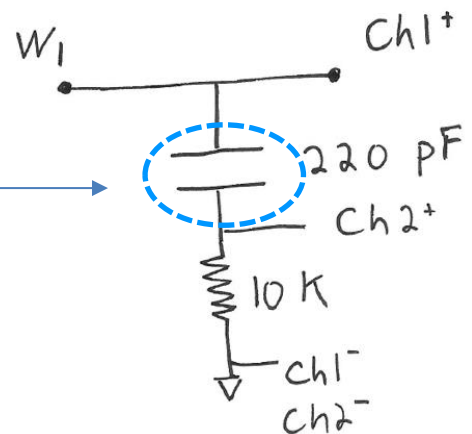

2. Connect the Discovery to your circuit.




Ensure the Discovery and circuit share a ground.

Use Wavegen 1 as the V_input

Use Scope Channel 1 to monitor V_input;

Use Scope Channel 2 to monitor the V dropped across the resistor.



3. Set  Wavegen , then ► Run

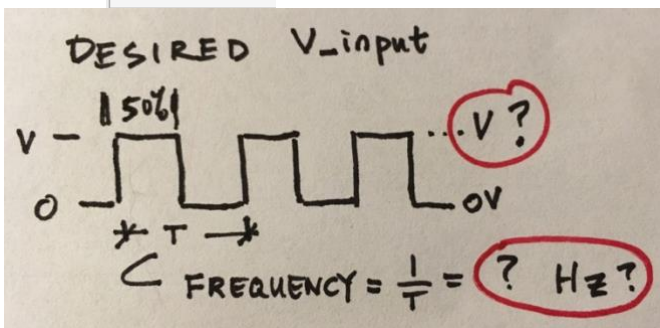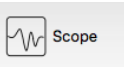






We want to set the V_input so that the humidity sensor will respond with the manufacturer's *reference curve*.

What *circuit conditions* (signal Hz, V_input) should we use?

Once you have determined the conditions for the waveform, ► Run


4. Set up , then 

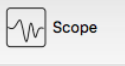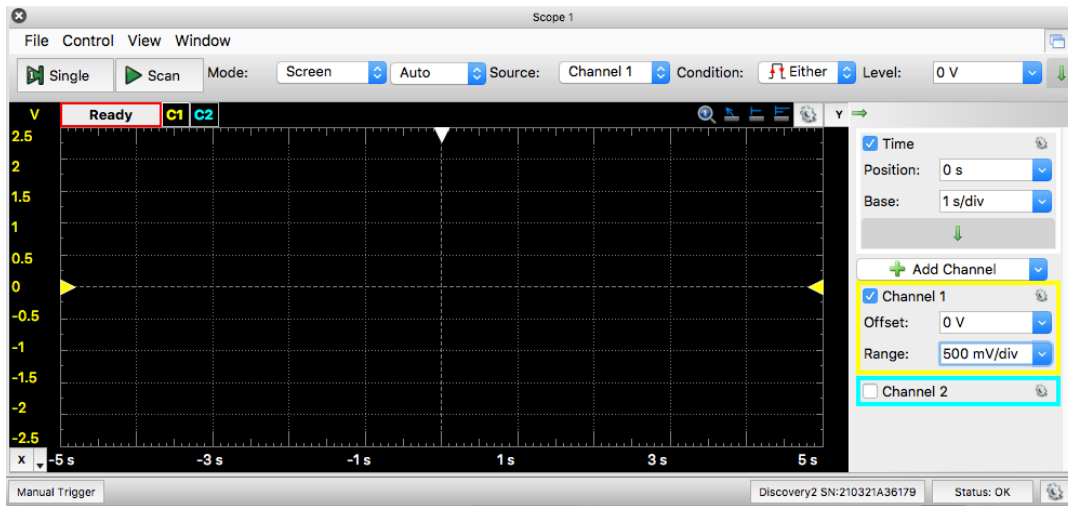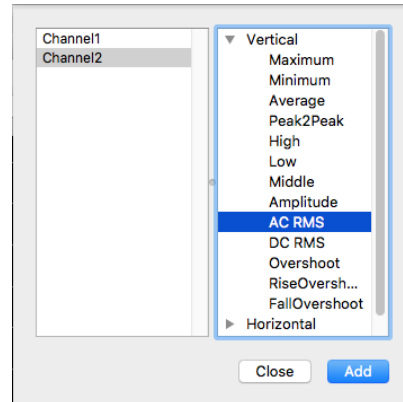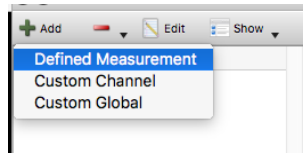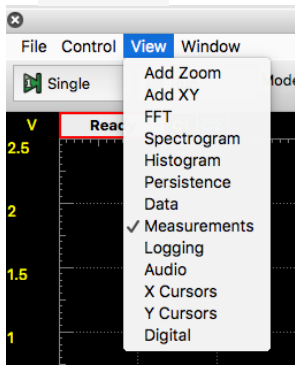In , add a measurement of Channel 2 Amplitude.



How can you adjust the time base to see 3-4 cycles?

Use Channel 2: What V range will allow you to see your input signal?

 Scan and complete the table below for your calibration curve

Capacitance value (R=10K)	Measured RMS Voltage amplitude
100 pF	
120 pF	
150 pF	
180 pF	
220 pF	

Once you have recorded the measurements (V-RMS), replace the 220 pF capacitor with a 100 pF capacitor. Note that the signal decays faster and the RMS voltage has decreased significantly. *How does this circuit feature help you with the goal of measuring humidity?*

Generate the plot of the C v. V-RMS relationship for your lab report from your measured data.

Part 2. Measuring the ambient %RH using your circuit



Replace the capacitor in your circuit with the [humidity sensor](#). **Take the measurement of the RMS amplitude.** From your calibration data from Part 1, and the data sheet for the [humidity sensor](#), determine the relative humidity of the room.

Check your result to the relative humidity of the day (which you can check at www.weather.com).

Deliverables:

The results you need to save are highlighted in **RED** in the lab above, just to help remind you as you go along what to save. The summary is listed below.

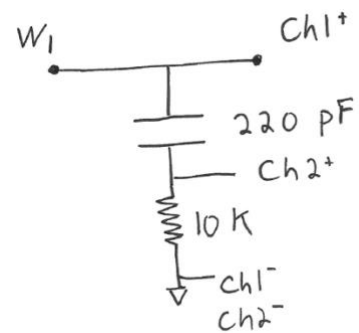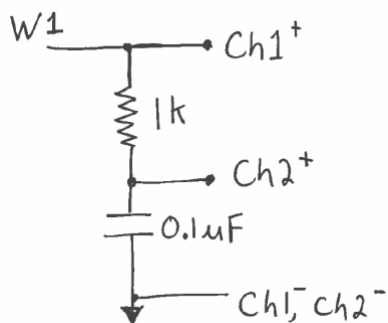- Plot the measured voltage versus time data from the 1 volt square wave at 10 kHz into the CR circuit.
- Comment on the difference with the RC circuit from last class.



- Compare your measurement to the *analytical solution*. Note that the analytical solution will be the same for the CR circuit as the RC circuit in the book, just with a minor adjustment.
- Plot your calibration data for the capacitance meter that you created (i.e. a plot of the table data). Plot a reasonable linear fit, overlaid on the data points and report what your calibration equation is.
- Report on your results of using the capacitance meter you built in Part 2 to measure the relative humidity. Check the humidity for the day and see if the result makes sense.

**analytical solution* = The value that you would get if you used the equations for an idealized RC or CR circuit.