# Problem set: RC circuits as signal filters—the Bode plot

<u>Goal:</u> Build and characterize the filtering behavior of two different filter circuits over a range of frequencies.



Source: http://www.chenyang.de/Signalprocessing.htm

Testing the RC filter and its behavior

#### Why do we want to filter signals?

Raw signals can contain the information disguised by noise or other unwanted information. Filters can help us to get rid of some of the information in the signal that we're not interested in.

A filter can be built from different combinations of resistors and capacitors.

What type of signal was filtered out from the original signal? How do you know?

**1.** Build the RC circuit shown; it will *filter* the input signal.

W1

**2.** Connect the Discovery to your circuit.



Ensure the Discovery and circuit share a ground.

Use Wavegen 1 as the V input signal.

Use Scope Channel 1 to monitor the input signal;

Use Scope Channel 2 to monitor the V dropped across the capacitor; we will consider this the *filter* output.



, then 闲 un



Waveger

3. Set

Choose a signal input frequency that will give you a sine wave period,  $T \cong RC$  circuit time constant,  $\tau$  ("tau").

The sine function takes an argument in units of radians\*.

How do you convert cycles/second (Hz) to radians/second ( $\omega$ ) for the **sin** function?

[This animation illustrates Hz  $\rightarrow \omega$ : How many  $\pi$  are in a complete a cycle?]

When you've set up the signal, Run

\*But Wavegen displays the **sin** wave in Hz.

Problem set: RC filters & the Bode Plot

3			_	_	_	Scope	91		_	_		
File	Control	View W	indow									6
<b>)</b>	Single	🕨 Scan	Mode:	Screen	Auto	Source:	Channel 1	Condition:	F Rising	Level:	0 V	<b>_</b> ↓
V	Rea	dy <mark>C1</mark>	C2					0 ⊾ ⊨	🗄 🚳 🛛	<b>→</b>		
.5	Demo	mode								🗹 Time		8
	[									Position:	0 s	
									1	Base:	100 ms/div	~
.5											ţ	
										🕂 🕂 Ad	d Channel	~
-										🗹 Channe	1	8
										Offset:	0 V	
										Range:	500 mV/div	~
0.5										🗹 Channe	12	8
										Offset:	0 V	
1	-									Range:	500 mV/div	~
1.5												
•												
2	-											
2.5	Ē			. <u></u>	İİ							
×	500 ms		-300 ms	-1	00 ms	100 ms	300	ms	500 ms			

How can you adjust the time base to see 3-4 cycles?

What V range will allow you to see your input signal?

# **5.** Test the circuit: Change the input frequency and notice the response

1 ...

. .



Adjust the frequency of the waveform to be ~10x lower- and ~10x higherthan the characteristic frequency of the filter given by RC.

Observe how the filter behaves qualitatively at both low- and highfrequencies.

Notice the amplitude of the output as well as the shift in time,  $\Delta t$ , between input signal and the output signal.

If your circuit is working as expected, it will allow some frequencies to pass through to V<sub>out</sub> and it will attenuate other frequencies?

Check with someone else. Are your circuits responding similarly?

#### 6. Measure and quantify how this RC circuit *responds* to different frequency inputs

We will model the input to the RC circuit as a sine wave:  $V_{in} = \sin(\omega t)$ , where  $\omega$  is the angular frequency in radians/second (also "rads/sec"). The output is expected to be  $V_{out} = A \cdot V_{in} \cdot \sin(\omega t + \phi)$ . From the book, we know that output amplitude will be:

$$A = \frac{1}{\sqrt{1 + (RC\omega)^2}} = \text{voltage gain}^*$$

And the angular shift in phase is:

$$\phi = \operatorname{atan}(-RC\omega)$$



Fill in the table below for the experimental and expected values. If you use the tools in the upper right of the Waveforms display, you can measure values to compute the theoretical values (the data shown are fake).



In Waveforms, the data display in the *time* domain (seconds).

Frequency, Hz (cycles/s)	Angular frequency, ω (rad/s)	RCω (unitless)	A (theoretical)	A (measured)	Ф,theory (degrees)	Δt, shift (seconds)	Φ,measured (degrees)
100							
500							
1,000							
5,000							
10,000							

Looking at the values in the table above, what happens to a 10,000 Hz signal that goes into this circuit? What about a 100 Hz signal?

Talk to someone in the lab about your results. How does this RC circuit respond to input signals?

\*This might be too much information:  $A = \frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + (RC\omega)^2}}$  = voltage gain. The decibel (dB) was developed as a unit to measure *Power* gain, 1 dB = 10 log (A<sub>power</sub>). Because *P* = *IV* = *V*<sup>2</sup>/*R* = *I*<sup>2</sup>*R*, *Gain*<sub>Power</sub> = *Gain*<sup>2</sup><sub>Voltage</sub> = *Gain*<sup>2</sup><sub>Current</sub>

### **7.** Analyze the circuit behavior with

Network

Add a component in Wavegen. This component is a Waveform generator and Scope wrapped into one. It is going to do all the work you did by hand in step 6. It displays the frequency response of the circuit in what is called a <u>Bode plot</u>. The Bode plot is the plot of amplitude and phase as a function of frequency.

There is no need to change your circuit or Analog Discovery set up from the last step—it will use the same channels.



Export and plot the amplitude part of your data from the Network Analyzer. Superimpose your data from the table above on the Bode plot as data points.

Remember the experimental output will be in dB while the amplitude, A, is just the ratio of output voltage to input voltage. See the book for converting to (or from) dB.

8. Build and test a CR circuit by hand (step 6.) and with a Network Analyzer (step 7)



Problem set: RC filters & the Bode Plot

In this case the amplitude and phase results change from the previous example. The expected results for amplitude and phase are;

$$A = \frac{RC\omega}{\sqrt{1 + (RC\omega)^2}}$$
$$\phi = \operatorname{atan}\left(\frac{1}{RC\omega}\right)$$

Frequency, Hz (cycles/s)	Angular frequency, ω (rad/s)	RCω (unitless)	A (theoretical)	A (measured)	Φ,theory (degrees)	Δt, shift (seconds)	Φ,measured (degrees)
100							
500							
1,000							
5,000							
10,000							

Recreate the Bode plot using the Network Analyzer as you did with the previous circuit. Create the same plot as you did for the other filter.

**Deliverable:** You can just turn in two plots from this work. The plots should be well-labeled and clear. This is not a lab and no further explanation is needed.